

Temporary ID

Assignment : 1

Date _____

Page _____

L D 20TDSS122 | 20DCS103 ← Permanent ID

1. The resistance of a certain length of wire is 4.6 Ω at 20°C and 5.68 Ω at 80°C.

Determine, a) temperature co-efficient of resistance of the material of wire at 0°C, b) resistance of wire at 60°C.

$$\rightarrow \text{Here, Let } R_1 = 4.6 \Omega, t_1 = 20^\circ\text{C} \quad | \quad \alpha_0 = ? \\ R_2 = 5.68 \Omega, t_2 = 80^\circ\text{C} \quad | \quad R_{60} = ?$$

$$\text{From, } R = R_0 (1 + \alpha_0 t) \quad \text{--- (1)}$$

$$\therefore \frac{R_1}{R_2} = \frac{R_0 (1 + \alpha_0 t_1)}{R_0 (1 + \alpha_0 t_2)}$$

$$\therefore \frac{R_1}{R_2} = \frac{1 + \alpha_0 t_1}{1 + \alpha_0 t_2}$$

$$\therefore R_1 + R_1 \alpha_0 t_2 = R_2 + R_2 \alpha_0 t_1$$

$$\therefore \alpha_0 (R_1 t_2 - R_2 t_1) = R_2 - R_1$$

$$\therefore \alpha_0 = \frac{R_2 - R_1}{R_1 t_2 - R_2 t_1} \\ = \frac{5.68 - 4.6}{(4.6)(80) - (5.68)(20)} \\ = 1.08$$

$$= 368 - 113.6$$

$$\therefore \alpha_0 = 0.00425 \text{ } ^\circ\text{C}^{-1}$$

→ To find resistance of wire at 60°C,

$$\frac{R_{60}}{R_{20}} = \frac{1 + \alpha_0(60)}{1 + \alpha_0(20)} \quad (\because \text{eq. (1)})$$

$$\therefore R_{60} = (4.6) \left[1 + (0.00425)(60) \right] \\ \left[1 + (0.00425)(20) \right]$$

$$\therefore R_{60} = \frac{5.773}{1.085} \quad \therefore R_{60} = 5.32 \Omega$$

2. The resistance of a wire of 3 mm^2 cross sectional area and 6 m length is 0.15Ω at 0°C . When the temperature of the wire is raised to 65°C the resistance is found to be 0.2Ω . Calculate the temperature coefficient of resistance of the wire and its resistivity at 0°C .

$$\rightarrow \text{Here, let } R_1 = 0.15 \Omega, t_1 = 0^\circ\text{C}, l = 6 \text{ m}$$

$$R_2 = 0.2 \Omega, t_2 = 65^\circ\text{C}, \alpha_0 = ?$$

$$A = 3 \text{ mm}^2 = 3 \times 10^{-6} \text{ m}^2, \rho_0 = ?$$

$$\rightarrow \text{From, } R = R_0(1 + \alpha_0 t)$$

$$\frac{R_1}{R_2} = \frac{R_0[1 + \alpha_0 t_1]}{R_0[1 + \alpha_0 t_2]}$$

$$\therefore \frac{R_1}{R_2} = \frac{1 + \alpha_0 t_1}{1 + \alpha_0 t_2}$$

$$\therefore R_1 + R_1 \alpha_0 t_2 = R_2 + R_2 \alpha_0 t_1$$

$$\therefore \alpha_0 (R_1 t_2 - R_2 t_1) = R_2 - R_1$$

$$\therefore \alpha_0 = \frac{R_2 - R_1}{R_1 t_2 - R_2 t_1}$$

$$= \frac{0.2 - 0.15}{(0.15)(65) - (0.2)(0)}$$

$$= \frac{0.05}{9.75}$$

$$\therefore \alpha_0 = 0.0051 \text{ } {}^\circ\text{C}^{-1}$$

$$\rightarrow \text{From, } R = \frac{\rho L}{A} \quad \rho_0 = \frac{R_0 A}{l}$$

$$\text{Where, } R_0 = 0.15, A = 3 \times 10^{-6} \text{ m}^2, l = 6 \text{ m}$$

Temporary ID

20TDCS122

Permanent ID

20DCCS103

 Date _____
 Page _____

$$\therefore \rho_0 = \frac{R_0 A}{l} = \frac{0.15 \times 3 \times 10^{-6}}{6} = 0.075 \times 10^{-6} \Omega \cdot \text{m}$$

$$\therefore \rho_0 = 7.5 \times 10^{-8} \Omega \cdot \text{m}$$

3. A copper wire has a resistivity of $1.6 \times 10^{-6} \Omega \cdot \text{cm}$ at 0°C and at 20°C , the temperature co-efficient of resistance is $\frac{1}{254.5} \cdot \text{C}^{-1}$. Find the resistivity and

temperature co-efficient of resistance at 60°C .

→ Here, $\rho_0 = 1.6 \times 10^{-6} \Omega \cdot \text{cm}$, $\alpha_{20} = \frac{1}{254.5} \cdot \text{C}^{-1}$

$$= 1.6 \times 10^{-8} \Omega \cdot \text{m}$$

$$\rho_{60} = ? \quad , \quad \alpha_{60} = ?$$

→ First we need to find α_0 ,
from $\alpha_t = \frac{\alpha_0}{1 + \alpha_0 t}$ — (1)

$$\alpha_{20} = \frac{\alpha_0}{1 + \alpha_0 \cdot 20}$$

$$\therefore \alpha_{20} + \alpha_{20} \cdot \alpha_0 \cdot 20 = \alpha_0$$

$$\therefore \alpha_0 (\alpha_{20} \cdot 20 - 1) = -\alpha_{20}$$

$$\therefore \alpha_0 = \frac{-\alpha_{20}}{\alpha_{20} \cdot 20 - 1} = \frac{\alpha_{20}}{1 - 20 \cdot \alpha_{20}}$$

$$\therefore \alpha_0 = \frac{1/254.5}{1 - 20 \cdot (1/254.5)}$$

$$\therefore \alpha_0 = 4.27 \times 10^{-3} \cdot \text{C}^{-1}$$

→ Now, $\rho_{60} = \rho_0 (1 + \alpha_0 \cdot 60)$

$$= 1.6 \times 10^{-8} (1 + (4.27 \times 10^{-3})(60))$$

$$\therefore \rho_{60} = 2.01 \times 10^{-8} \Omega \cdot \text{m}$$

Temporary ID

20TDCS122

Permanent ID

20DCS103

Date _____
Page _____

→ And now again from eq. (1),



$$\alpha_{60} = \frac{\alpha_0}{1 + \alpha_{0t}} = \frac{4.27 \times 10^{-3}}{1 + (4.27 \times 10^{-3})(60)} = 4.27 \times 10^{-3}$$

1.2562

$$= 3.399 \times 10^{-3} \text{ } ^\circ\text{C}^{-1}$$

$$\therefore \alpha_{60} = \frac{1}{294.2} \text{ } ^\circ\text{C}^{-1}$$

4. Find the current supplied by the battery in the network shown below in figure-1 by using star delta transformation.

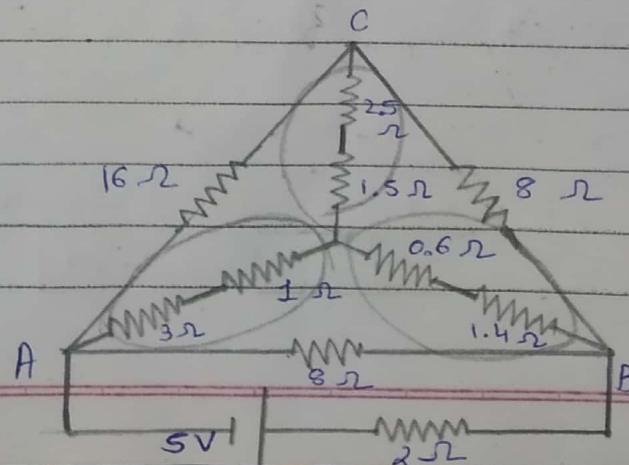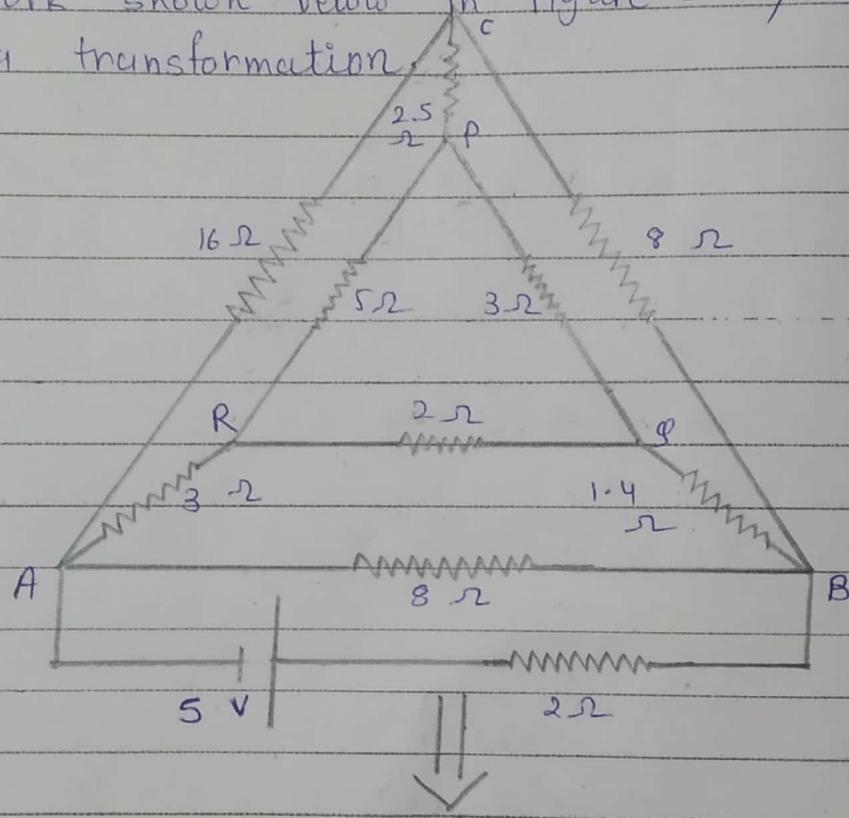

Temporary ID

20TDCS 122

Permanent ID

20DCS103




→ Here, let $R_{PG} = 3 \Omega$, $R_{GR} = 2 \Omega$, $R_{PR} = 5 \Omega$

$$\therefore R_p = \frac{R_{PG} R_{PR}}{R_{PG} + R_{GR} + R_{PR}} = \frac{3 \times 5}{3 + 2 + 5} = 1.5 \Omega$$

$$\therefore R_g = \frac{R_{PG} R_{PG}}{R_{PG} + R_{GR} + R_{PR}} = \frac{3 \times 2}{3 + 2 + 5} = 0.6 \Omega$$

$$\therefore R_r = \frac{R_{PR} * R_{GR}}{R_{PG} + R_{GR} + R_{PR}} = \frac{5 \times 2}{3 + 2 + 5} = 1 \Omega$$

→ After substituting series connections,
we get...

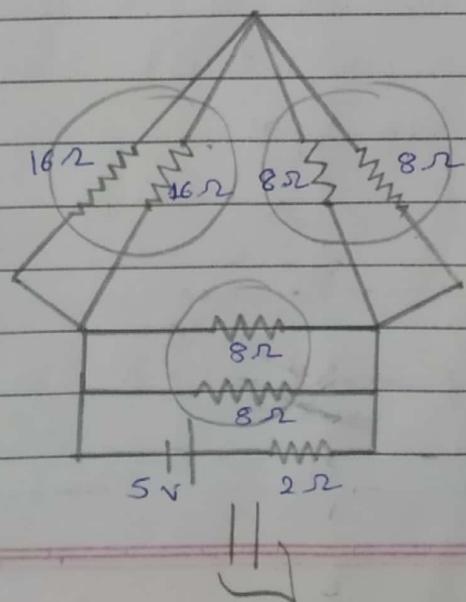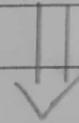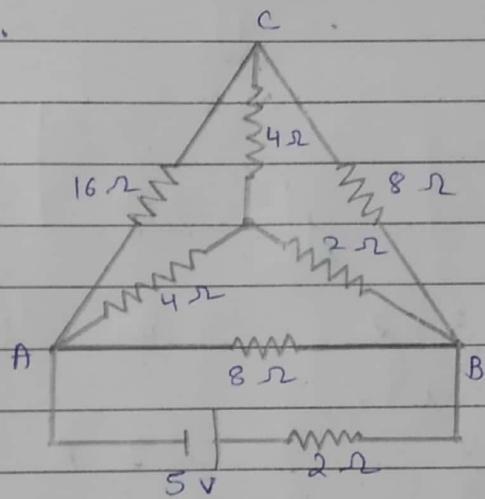


Temporary ID
20TDCS122

Permanent ID
20DCS103

Date _____

Page _____

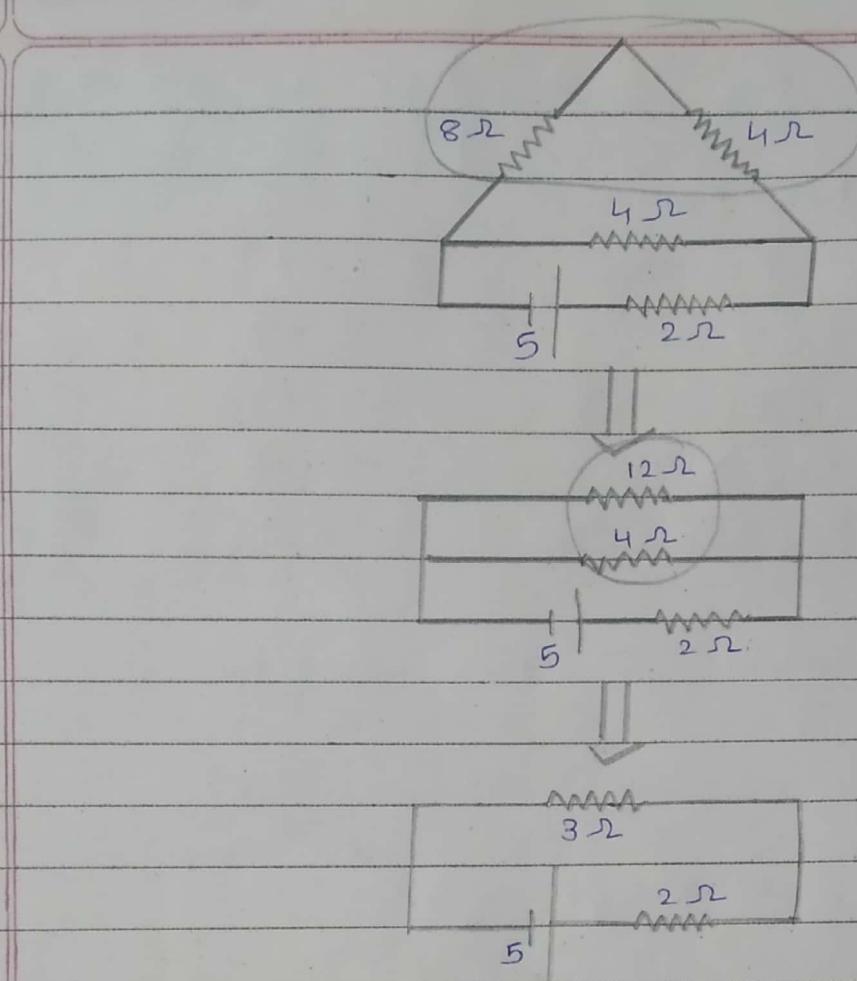


→ Here, $R_{eq} = 3 + 2 = 5 \Omega$ & $V = 5V$.
→ For the current,

$$I = \frac{V}{R} = \frac{5}{5} = 1 A$$

$$\therefore I = 1 A$$

5. Determine equivalent resistance between terminal A and B shown in network (figure-2) by using star delta transformation.

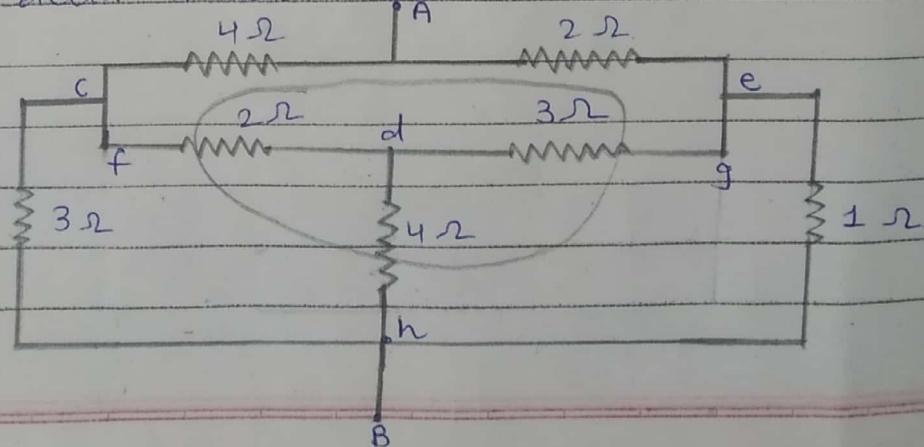


Temporary ID

20TDCS122

Permanent ID

20DCS103

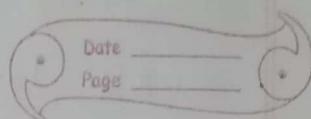


→ Star to delta transformation :-

$$\text{let, } R_f = 2\ \Omega, R_g = 3\ \Omega, R_h = 4\ \Omega.$$

$$\therefore R_{fg} = 2 + 3 + \frac{2 \times 3}{4} = 5 + 1.5 = 6.5\ \Omega.$$

$$\therefore R_{fh} = 2 + 4 + \frac{2 \times 4}{3} = 6 + \frac{8}{3} = 8.67\ \Omega$$
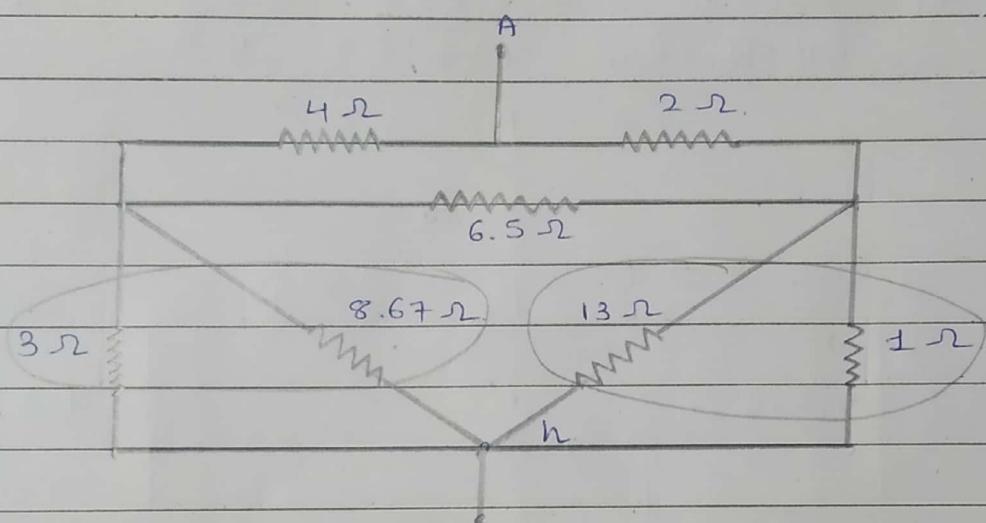
$$\therefore R_{gh} = 3 + 4 + \frac{3 \times 4}{2} = 7 + 6 = 13\ \Omega.$$



→ Here, L.H.S. 3 Ω and 8.67 Ω are in parallel,


$$\therefore \frac{1}{R_{xc}} = \frac{1}{3} + \frac{1}{8.67} = \frac{8.67 + 3}{8.67 \times 3}$$

$$\therefore R_{xc} = \frac{26.01}{11.67} = 2.228\ \Omega$$

& R.H.S. 13 Ω and 1 Ω are in parallel,

$$\therefore \frac{1}{R_y} = \frac{1}{1} + \frac{1}{13} = \frac{13 + 1}{13}$$

$$\therefore R_y = \frac{13}{14} = 0.928\ \Omega$$

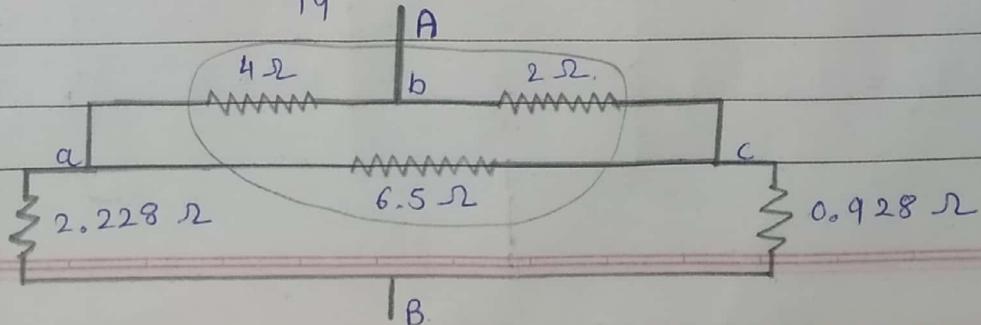

Temporary ID

20TDCS122

Permanent ID

20DCS103

Date _____

Page _____


→ Now, Delta to star conversion :-

Let $R_{ab} = 4 \Omega$, $R_{bc} = 2 \Omega$, $R_{ca} = 6.5 \Omega$

$$\therefore R_a = \frac{R_{ab} \cdot R_{ac}}{R_{ab} + R_{bc} + R_{ca}} = \frac{4 \times 6.5}{4 + 2 + 6.5} = \frac{26}{12.5} = 2.08 \Omega$$

$$\& R_b = \frac{R_{ab} R_{bc}}{R_{ab} + R_{bc} + R_{ca}} = \frac{4 \times 2}{4 + 2 + 6.5} = \frac{8}{12.5} = 0.64 \Omega$$
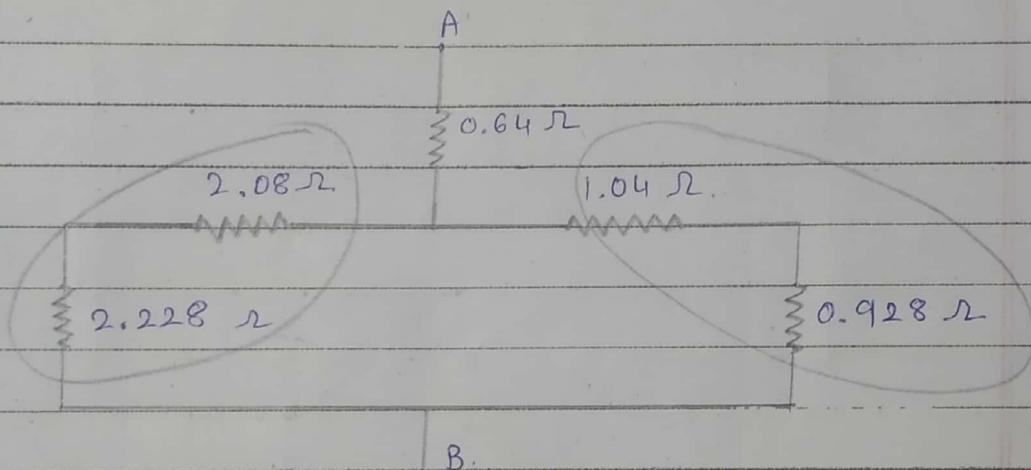
$$\& R_c = \frac{R_{ac} R_{bc}}{R_{ab} + R_{bc} + R_{ca}} = \frac{6.5 \times 2}{4 + 2 + 6.5} = \frac{13}{12.5} = 1.04 \Omega$$




→ Here, 2.08Ω and 2.228Ω are in series connection,

$$\therefore R_L = 2.08 + 2.228 = 4.308 \Omega$$

and 1.04Ω and 0.928Ω are in series connection,

$$\therefore R_p = 1.04 + 0.928 = 1.968 \Omega$$

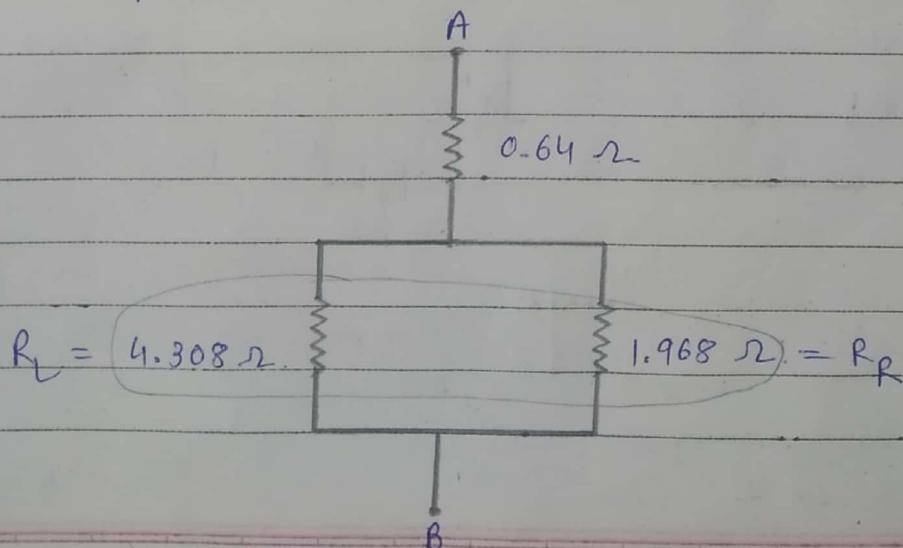

Temporary ID.

20TDCS122

Permanent ID

20DCS103

Date _____

Page _____

→ Here, R_L & R_p is in parallel connection,

$$\therefore R_{RL} = \frac{4.308 \times 1.968}{4.308 + 1.968} = \frac{8.478}{6.276} = 1.35 \Omega$$

→ R_{RL} is in series connection with 0.64Ω

$$\therefore R_{eq} = 0.64 + 1.35$$




$$\therefore R_{eq} = 1.99 \Omega$$

6. Determine current in $xx \Omega$ resistor shown in network by using star-delta transformation.

→ My ID. 20DCS103 (Permanent)

→ My ID. 20TDCS122 (Temporary)

→ Here, $xx = 122 \Omega$

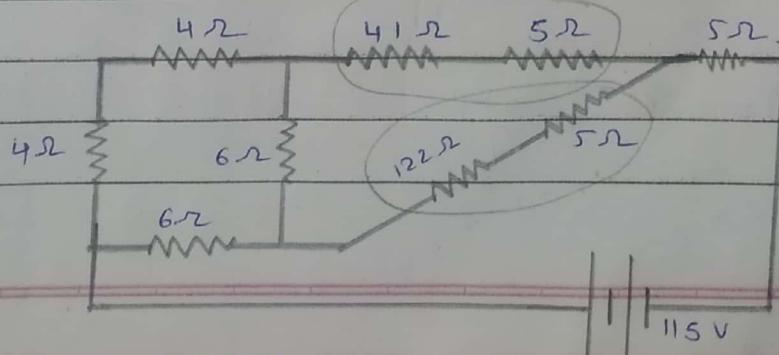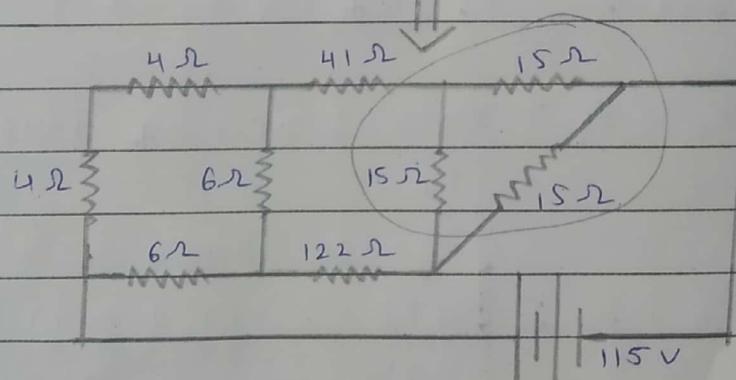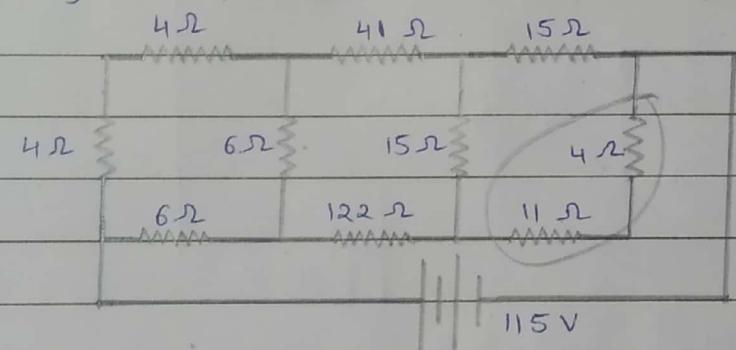

Temporary ID
20TDCS122

Permanent ID
20DCS103

Date _____
Page _____

→ Here, all three resistance are $15\ \Omega$.

Delta to star transformation,

$$R = \frac{15 \times 15}{15 + 15 + 15} = \frac{225}{45} = 5\ \Omega$$


∴ We can put the value $5\ \Omega$ to all three star transformed resistance.

→ And $41\ \Omega$ & $5\ \Omega$ and $122\ \Omega$ & $5\ \Omega$ are in series connection.

$$R_a = 41 + 5 = 46\ \Omega$$

$$\& R_b = 122 + 5 = 127\ \Omega$$

Then we can get,

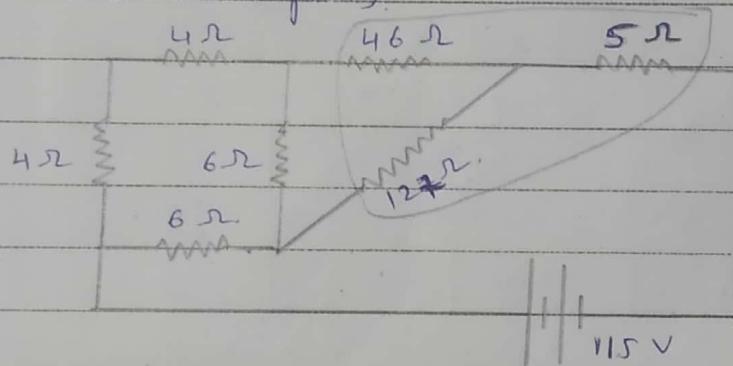

→ Star to delta connection...

$$\text{Let } R_{ab} = 46\ \Omega, R_b = 127\ \Omega, R_c = 5\ \Omega.$$

$$\& R_{ab} = R_a + R_b + \frac{R_a R_b}{R_c} = 46 + 127 + \frac{(46)(127)}{5}$$
$$= 1341.4\ \Omega$$

$$\& R_{bc} = R_b + R_c + \frac{R_b R_c}{R_a} = 127 + 5 + \frac{(127)(5)}{46}$$
$$= 145.8\ \Omega$$

$$\& R_{ac} = R_a + R_c + \frac{R_a R_c}{R_b} = 46 + 5 + \frac{(46)(5)}{127}$$
$$= 52.81\ \Omega$$


Temporary ID

20 TDCS102

Permanent ID

20 DCS103

Date _____
Page _____

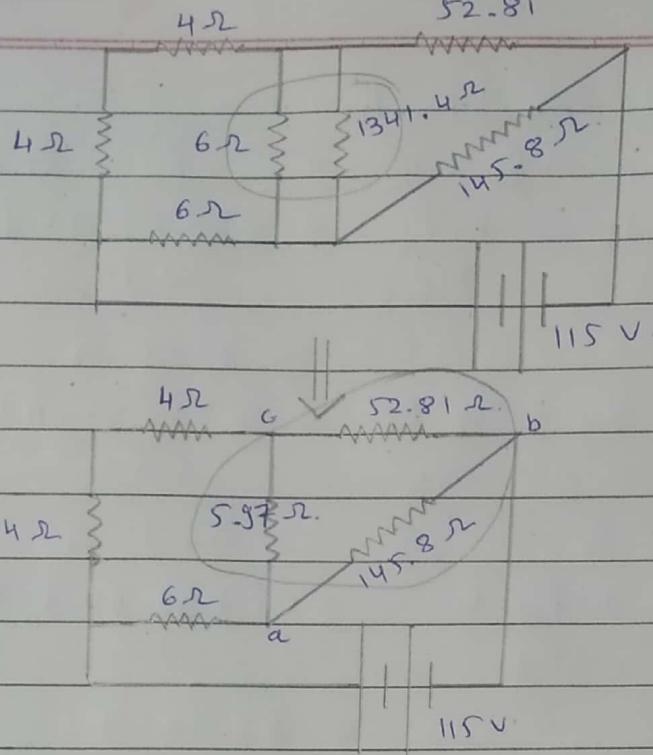


→ Delta to star transformation...


$$R_a = \frac{R_{ab} + R_{ac}}{R_{ab} + R_{bc} + R_{ca}} = \frac{145.8 + 52.81}{145.8 + 52.81 + 5.97} = 37.64 \Omega$$

$$R_b = \frac{R_{ab} + R_{bc}}{R_{ab} + R_{bc} + R_{ca}} = \frac{145.8 + 5.97}{145.8 + 52.81 + 5.97} = 4.25 \Omega$$
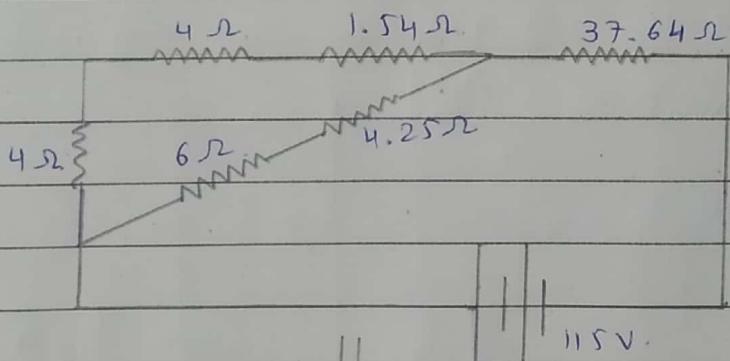
$$R_c = \frac{R_{ac} + R_{bc}}{R_{ab} + R_{bc} + R_{ca}} = \frac{52.81 + 5.97}{145.8 + 52.81 + 5.97} = 1.54 \Omega$$



→ (Refer)

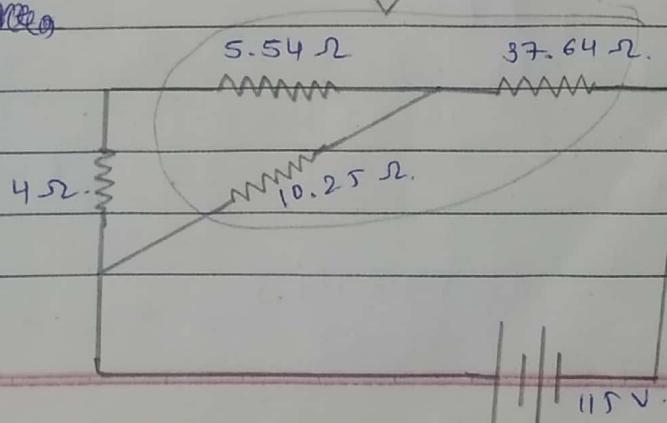

Temporary ID

20TDCS122

Permanent ID

20DCCS103

Date _____

Page _____

→ Star to delta transformation :-

$$\text{let } R_a = 5.54 \Omega, R_b = 10.25 \Omega, R_c = 37.64 \Omega$$

$$\therefore R_{ab} = R_a + R_b + \frac{R_a R_b}{R_c} = \frac{5.54 \times 10.25 + 5.54 + 10.25}{37.64}$$

$$= 17.3 \Omega.$$


$$\& R_{bc} = R_b + R_c + \frac{R_b \cdot R_c}{R_a} = \frac{10.25 \times 37.64 + 10.25 + 37.64}{5.54}$$

$$= 117.5 \Omega$$


$$\& R_{ca} = R_a + R_c + \frac{R_a \cdot R_c}{R_b} = \frac{5.54 + 37.64 + 5.54 \times 37.64}{10.25}$$

$$= 63.52 \Omega$$

→ Now, we can get ...

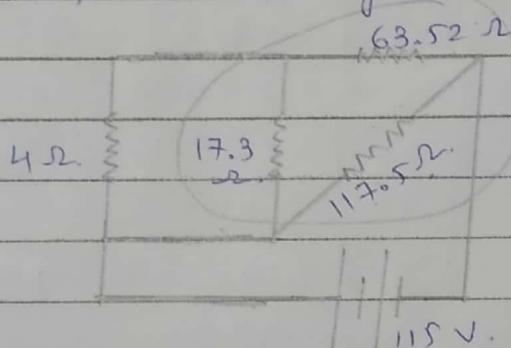

Delta to star transformation

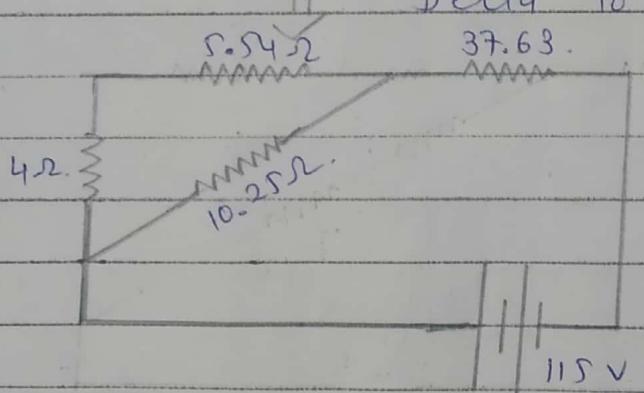

→ fig. (e)

$$\text{let } R_{ab} = 17.3 \Omega, R_{bc} = 63.52 \Omega, R_{ca} = 117.5 \Omega.$$

$$R_a = \frac{R_{ab} + R_{ac}}{R_{ab} + R_{bc} + R_{ca}} = \frac{17.3 + 117.5}{17.3 + 63.52 + 117.5} = \frac{2032.75}{198.32} = 10.25 \Omega$$


$$R_c = \frac{R_{bc} + R_{ca}}{R_{ab} + R_{bc} + R_{ca}} = \frac{63.52 + 117.5}{198.32} = 37.63 \Omega$$

Temporary ID

Permanent ID

20TDCS122

20DCS103

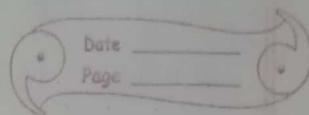

$$R_b = \frac{R_{ab} \cdot R_{bc}}{R_{ab} + R_{bc} + R_{ca}} = \frac{17.3 \Omega \times 63.5 \Omega}{198.32} = 5.54 \Omega$$

- From figure (*) 4Ω & 5.54Ω are in series connection.
 $\therefore R$ will be $4 + 5.54 = 9.54 \Omega$.

which is parallel to 10.25Ω

$$\therefore \frac{1}{R_L} = \frac{1}{10.25} + \frac{1}{9.54} \Omega$$

$$\therefore R_L = \frac{10.25 \times 9.54}{10.25 + 9.54} = \frac{97.785}{19.79} = 4.94 \Omega$$

- Then R_L will be in series with ~~4.94Ω~~ . 37.63Ω .

$$\therefore R_{eq} = 37.63 + 4.94$$



$$\therefore R_{eq} = 42.57 \Omega$$

- To determine the current,

$$I = \frac{V}{R} = \frac{115}{42.57} = 2.70 A$$

$$\therefore I = 2.70 A.$$

7. For the circuit, determine the voltage across the 20Ω resistor using mesh analysis.

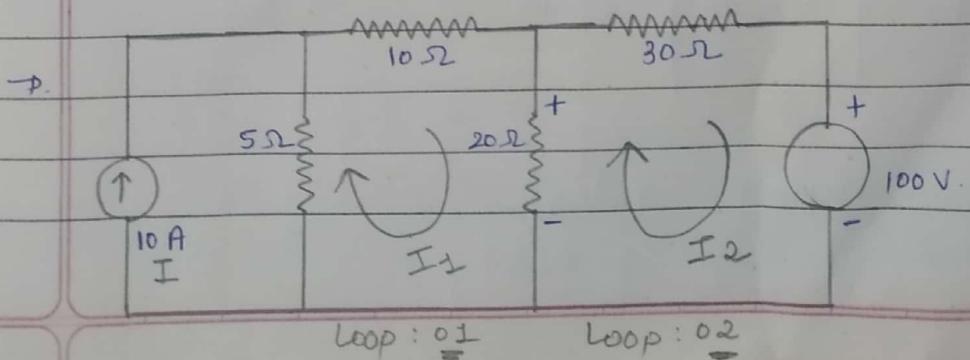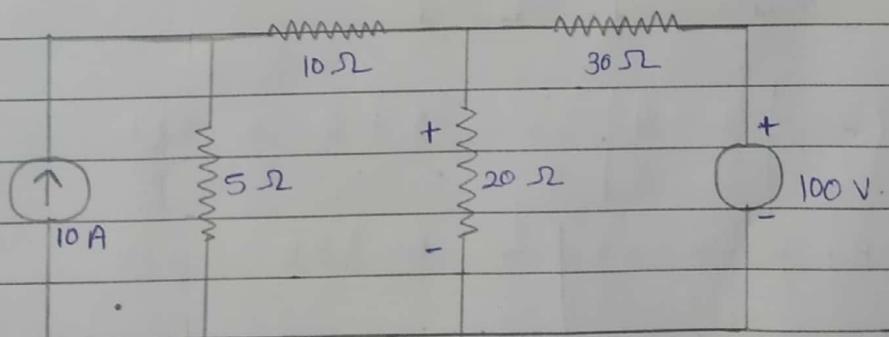


Temporary ID

20TDCS122

Permanent ID

20DCS103

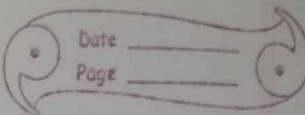

→ Here, $I = 10 \text{ A}$

Now, applying KVL to loop: 01,

$$-10I_1 - 20(I_1 - I_2) - 5(I_1 - I) = 0.$$

$$\therefore -10I_1 - 20I_1 + 20I_2 - 5I_1 + 5I = 0$$

$$\therefore -35I_1 + 20I_2 + 5(10) = 0$$

$$\therefore 35I_1 - 20I_2 = 50$$

$$\therefore 7I_1 - 4I_2 = 10 \quad \text{--- (1)}$$

Now, applying KVL to loop: 02,

$$-100 - 20(I_2 - I_1) - 30I_2 = 0.$$

$$\therefore -20I_2 + 20I_1 - 30I_2 = 100$$

$$\therefore 20I_1 - 50I_2 = 100$$

$$\therefore 2I_1 - 5I_2 = 10 \quad \text{--- (2)}$$

→ From eq. (1) and (2),

$$\begin{bmatrix} 7 & -4 \\ 2 & -5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 10 \\ 10 \end{bmatrix}$$

$$\text{Now, } \Delta R = \begin{vmatrix} 7 & -4 \\ 2 & -5 \end{vmatrix} = -35 + 8 = -27$$

$$\Delta R_1 = \begin{vmatrix} 10 & -4 \\ 10 & -5 \end{vmatrix} = -50 + 40 = -10.$$

$$\Delta R_2 = \begin{vmatrix} 7 & 10 \\ 2 & 10 \end{vmatrix} = 70 - 20 = 50.$$

→ Now, using cramer's rule,

$$I_1 = \frac{\Delta R_1}{\Delta R} = \frac{-10}{-27} = 0.37$$

Temporary ID

20TDCS122

Permanent ID

20DCS103

Date _____
Page _____

$$I_2 = \frac{\Delta R_2}{\Delta R} = \frac{50}{-27} = -1.85$$

→ Current through $20\ \Omega$ is $I_1 - I_2$
 $= 0.37 - (-1.85)$


$$I_x = 2.22\ A$$

& voltage across $20\ \Omega$ is $V = I_x R$

$$= 2.22 \times 20$$


$$\therefore V = 44.4\ V$$

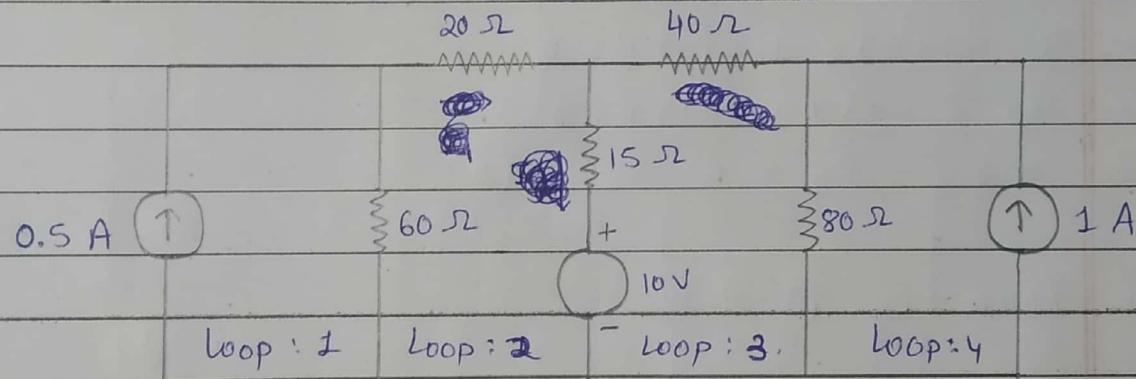8. Using mesh analysis find currents I_1 , I_2 , and I_3 for given circuit.



→ Here, $I_L = 0.5\ A$, $I_R = 1\ A$

Now, Applying KVL to loop 1,

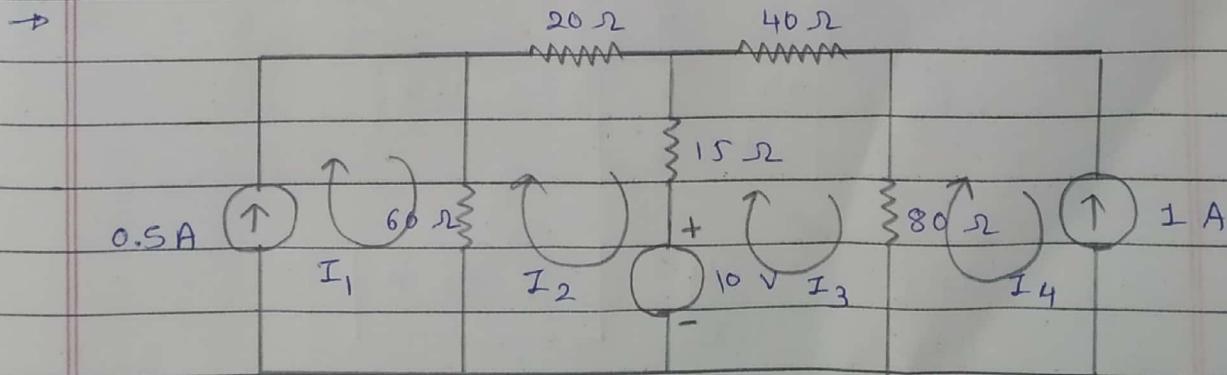

Temporary ID

20TDCS122

Permanent ID

20TDCS103

Date _____

Page _____

→ Now, applying KVL to loop : 2,

$$-20I_2 - 15(I_2 - I_3) - 10 - 60(I_2 - 0.5) = 0$$

$$\therefore -20I_2 - 15I_2 + 15I_3 - 10 - 60I_2 + 30 = 0$$

$$\therefore -95I_2 + 15I_3 = -20$$

$$\therefore 20 = 95I_2 - 15I_3$$

$$\therefore 4 = 19I_2 - 3I_3 \quad \text{--- (1)}$$

& applying KVL to loop : 3,

$$-40I_3 - 80(I_3 - 1) + 10 - 15(I_3 - I_2) = 0$$

$$\therefore -40I_3 - 80I_3 + 80 + 10 - 15I_3 + 15I_2 = 0.$$

$$\therefore 90 - 135I_3 + 15I_2 = 0$$

$$\therefore 90 = -15I_2 + 135I_3$$

$$\therefore 9I_3 - I_2 = 6 \quad \text{--- (2)}$$

→ From eq. (1) & (2),

$$\begin{bmatrix} 19 & -3 \\ -1 & 9 \end{bmatrix} \begin{bmatrix} I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 4 \\ 6 \end{bmatrix}$$

$$\therefore \text{Now, } \Delta R = \begin{vmatrix} 19 & -3 \\ -1 & 9 \end{vmatrix} = 168$$

$$\Delta R_2 = \begin{vmatrix} -4 & -3 \\ 6 & 9 \end{vmatrix} = 54$$

$$\Delta R_3 = \begin{vmatrix} 19 & 4 \\ -1 & 6 \end{vmatrix} = 118.$$

$$\therefore I_2 = \frac{\Delta R_2}{\Delta R} = \frac{54}{168} = 0.32 \text{ A.}$$


$$\therefore I_3 = \frac{\Delta R_3}{\Delta R} = \frac{118}{168} = 0.7$$

Temporary ID


20TDCS122

Permanent ID


20DCCS103

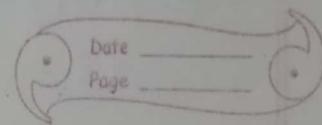

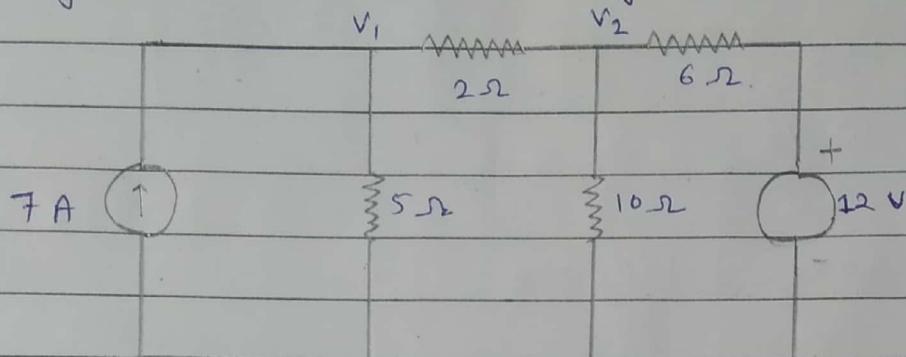9. For the circuit of figure-6 determine the nodal voltages and current through $2\ \Omega$ resistor.



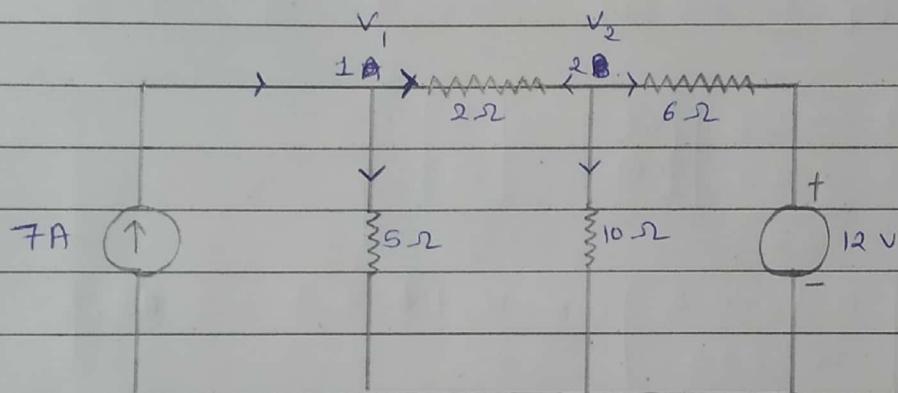→ Now, identifying the number of nodes in the given circuit.



→ Now, applying KCL at node 1,

$$\frac{v_1}{5} + \frac{v_1 - v_2}{2} = 7$$

$$\therefore 0.2v_1 + 0.5v_1 - 0.5v_2 = 7$$

$$\therefore 0.7v_1 - 0.5v_2 = 7 \quad \text{(1)}$$

→ Now, applying KCL at node 2,

$$\frac{v_2 - 12}{6} + \frac{v_2}{10} + \frac{v_2 - v_1}{2} = 0$$

$$\therefore \frac{v_2}{6} - 2 + \frac{v_2}{10} + \frac{v_2}{2} - \frac{v_1}{2} = 0.$$

Temporary ID
20TDCS122

Permanent ID
20DCCS103

Date _____
Page _____

$$\therefore \frac{V_2}{6} + \frac{V_2}{10} + \frac{5V_2}{10} - \frac{V_1}{2} = 2$$

$$\therefore \frac{10V_2 + 6V_2 + 30V_2}{60} - \frac{V_1}{2} = 2$$

$$\therefore \frac{46V_2}{60} - \frac{V_1}{2} = 2$$

$$\therefore \frac{23V_2}{30} - \frac{15V_1}{30} = 2$$

$$\therefore 23V_2 - 15V_1 = 60 \quad \text{--- (2)}$$

→ From eq. (1) & (2) ...

$$\begin{bmatrix} 0.7 & -0.5 \\ -15 & 23 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 7 \\ 60 \end{bmatrix}$$

$$\Delta R = \begin{vmatrix} 0.7 & -0.5 \\ -15 & 23 \end{vmatrix} = 16.1 \neq 7.5 = 8.6$$

$$\Delta R_1 = \begin{vmatrix} 7 & -0.5 \\ 60 & 23 \end{vmatrix} = 161 \neq 30 = 191$$

$$\Delta R_2 = \begin{vmatrix} 0.7 & 7 \\ -15 & 60 \end{vmatrix} = 42 + 105 = 147$$

$$\rightarrow \text{Now, } V_1 = \frac{\Delta R_1}{\Delta R} = \frac{191}{8.6} = 5.55.$$

$$\therefore V_1 = \frac{191}{8.6} = 22.2 \text{ V.}$$

$$\& V_2 = \frac{\Delta R_2}{\Delta R} = \frac{147}{8.6} = 17.1 \text{ V.}$$

Temporary ID

20TDCS122


Permanent ID

20DCS103

Date _____
Page _____

→ Current through 2Ω is $\frac{V_1 - V_2}{2} = \frac{22.2 - 17.1}{2}$
 $= \frac{5.04}{2}$
 $\therefore I = 2.55 A.$

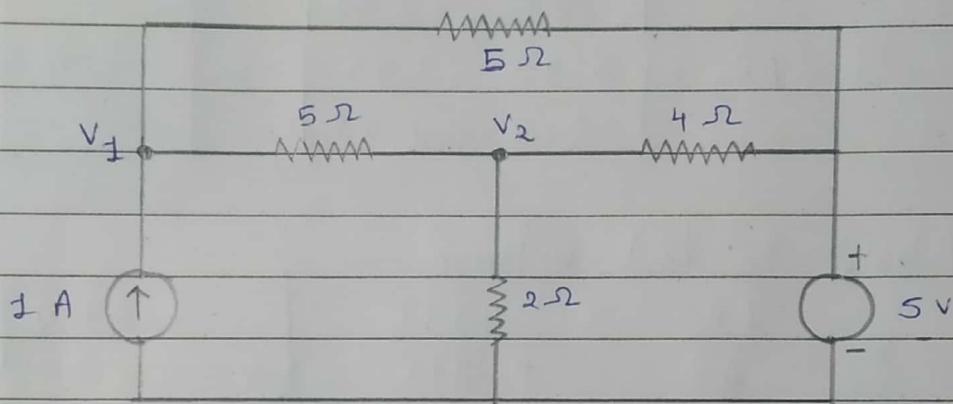10. For the circuit of figure determine the V_1 and V_2 nodal voltages.



→ Here, applying KCL to node 1,

$$\therefore I = \frac{V_1 - V_2}{5} + \frac{V_1 - 5}{20}$$

$$\therefore 1 = 0.2V_1 - 0.2V_2 + 0.05V_1 - 0.25$$

$$\therefore 1.25 = 0.25V_1 - 0.2V_2$$

(1)

Now, applying KCL to node 2,

$$\therefore 0 = \frac{V_2 - V_1}{5} + \frac{V_2 - 5}{4} + \frac{V_2}{2}$$

$$\therefore 0 = 0.2V_2 - 0.2V_1 + 0.25V_2 - 1.25 + 0.5V_2$$

$$\therefore 1.25 = 0.95V_2 - 0.2V_1$$

$$\therefore 1.25 = -0.2V_1 + 0.95V_2$$

(2)

Temporary ID

20TDCS122

Permanent ID

20DCS103

Date _____

Page _____

→ From eq. (1) and (2) ...

$$\begin{bmatrix} 0.25 & -0.2 \\ -0.2 & 0.95 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 1.25 \\ 1.25 \end{bmatrix}$$

$$\text{Now, } DR = \begin{vmatrix} 0.25 & -0.2 \\ -0.2 & 0.95 \end{vmatrix} = 0.1975$$

$$\& DR_1 = \begin{vmatrix} 1.25 & -0.2 \\ 1.25 & 0.95 \end{vmatrix} = 1.4375$$

$$\& DR_2 = \begin{vmatrix} 0.25 & 1.25 \\ -0.2 & 1.25 \end{vmatrix} = 0.5625$$

→ Now, To find voltage ...

$$V_1 = \frac{DR_1}{DR} = \frac{1.4375}{0.1975} = 7.27 \text{ V.}$$

$$V_2 = \frac{DR_2}{DR} = \frac{0.5625}{0.1975} = 2.85 \text{ V.}$$

→ Current through 5Ω is $\frac{V_1 - V_2}{5}$

$$= 7.27 - 2.85$$

5

$$I = 0.89 \text{ A}$$

11. Two metal plates of area 100 cm^2 are separated by a dielectric of 2 mm having a relative permittivity of 5. When a dc voltage of 500 V is applied across the capacitor plates, find
 (i) capacitance, (ii) charge on the capacitor,
 (iii) electric field strength, (iv) electric flux density.

Temporary ID

20TDCS122

Permanent ID

20DCS103

Date _____

Page _____

$$\rightarrow \text{Here, } A = 100 \text{ cm}^2 = 100 \times 10^{-4} \text{ m}^2 = 10^{-2} \text{ m}^2$$
$$d = 2 \text{ mm} = 2 \times 10^{-3} \text{ m}$$

$$\epsilon_0 = 5$$

$$V = 500 \text{ V}$$

(i) The capacitance, $C = \frac{\epsilon_0 A}{d}$

$$= \epsilon_0 \epsilon_0 A/d$$

$$\therefore C = \frac{8.85 \times 10^{-12}}{2 \times 10^{-3}} \times 10^{-2} \times 5$$

$$\therefore C = 22.125 \times 10^{-11}$$

$$\therefore C = 221.25 \text{ pF}$$

(ii) Charge on the capacitor, $q = CV$

$$\therefore q = 22.125 \times 10^{-11} \times 500$$
$$= 11062.5 \times 10^{-11}$$

$$\therefore q = 0.1107 \times 10^{-6} \text{ C}$$

(iii) Electric field strength, $E = \frac{V}{d}$

$$\therefore E = \frac{500}{2 \times 10^{-3}}$$
$$= 250 \times 10^3 \text{ V/m}$$

$$\therefore E = 250 \text{ kV/m}$$

(iv) Electric flux density, $D = \frac{q}{A}$

$$\therefore D = \frac{11062.5 \times 10^{-11}}{10^{-2}}$$

$$\therefore D = 0.1107 \times 10^{-4} = 11.07$$
$$\therefore D = 11.07 \times 10^{-6} \text{ C/m}^2$$

Temporary ID

20TIDCS122

Permanent ID

20DCS103

Date _____

Page _____


12. A capacitor is made up of two plates with an area of 11 cm^2 which are separated by a mica sheet 2 mm thick. If the relative permittivity of mica is 6 , find its capacitance. Now, if one plate is moved further to give an air gap 0.5 mm wide between the plate and mica, find the new capacitance.

 \rightarrow

$$A = 11 \text{ cm}^2 = 11 \times 10^{-4} \text{ m}^2$$

$$\epsilon_{r1} = 6$$
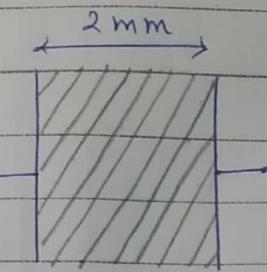
$$d = 2 \text{ mm} = 2 \times 10^{-3} \text{ m}$$



$$C_1 = \frac{\epsilon_r A}{d} = \frac{\epsilon_0 \epsilon_r A}{d}$$

$$= \frac{8.85 \times 10^{-12}}{2 \times 10^{-3}} \times 6 \times 11 \times 10^{-4}$$

$$= 292.05 \times 10^{-13}$$


$$= 29.2 \times 10^{-12}$$

$$\therefore C_1 = 29.2 \text{ pF.}$$

- \rightarrow . Now, one plate is moved farther...

$$\text{Here, } d_1 = 2 \times 10^{-3} \text{ m}$$

$$d_2 = 0.5 \times 10^{-3} \text{ m}$$

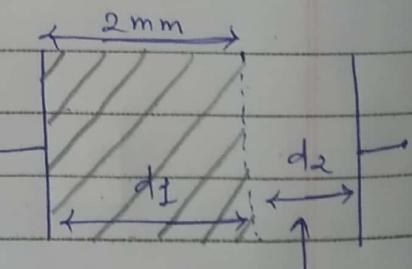

$$C_2 = \frac{\epsilon_0 A}{d_1 + d_2}$$

$$\frac{\epsilon_0}{\epsilon_{r1} \epsilon_{r2}}$$

$$= \frac{8.85 \times 10^{-12}}{\frac{2 \times 10^{-3}}{6} + \frac{0.5 \times 10^{-3}}{1}} \times 11 \times 10^{-4}$$

air gap

Temporary ID

20TDCS122

Permanent ID


20DLS103

Date _____
Page _____

$$\begin{aligned}\therefore C_2 &= \frac{97.35 \times 10^{-16} \times 6}{2 \times 10^{-3} + 3 \times 10^{-3}} \\ &= \frac{97.35 \times 6 \times 10^{-16}}{5 \times 10^{-3}} \\ &= 116.82 \times 10^{-13} \\ &= 11.68 \times 10^{-12} \\ \therefore C_2 &= 11.68 \text{ pF}\end{aligned}$$

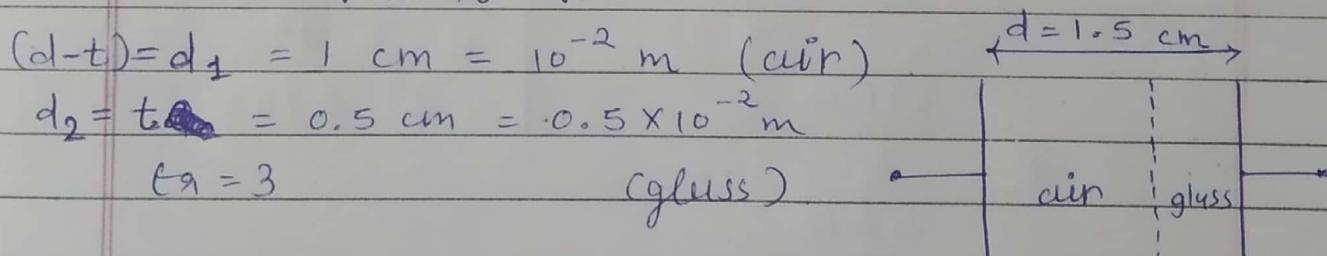13. Two plates are kept 1.5 cm apart in air and 2 kV supply is connected across them. Calculate the electric field strength in air when a glass sheet 0.5 cm thick with relative permittivity 3 is introduced between the plates without changing the previous distance between the plates.

→ Here, $d = 1.5 \text{ cm} = 1.5 \times 10^{-2} \text{ m}$
 $V = 10^3 \text{ V}$



→ $C = \frac{C_1 C_2}{C_1 + C_2}$

$$\therefore C = \frac{\epsilon_0 A}{d_1} \times \frac{\epsilon_0 \epsilon_r A}{d_2}$$

$$\frac{\epsilon_0 A}{d_1} + \frac{\epsilon_0 \epsilon_r A}{d_2}$$

$\therefore C = \frac{\epsilon_0 A}{d_1} \cdot \frac{\epsilon_0 \epsilon_r A}{d_2}$

$$\epsilon_0 \left(\frac{1}{d_1} + \frac{\epsilon_r}{d_2} \right)$$

Temporary ID

20TDCS122

Permanent ID

20DCS103

Date _____

Page _____

$$\therefore \frac{\phi}{V} = \frac{\epsilon_0 \epsilon_r A}{d_1 d_2}$$

$$\frac{1}{d_1} + \frac{\epsilon_r}{d_2}$$

$$\therefore \frac{\phi}{V} = \frac{\epsilon_0 \epsilon_r A}{d_1 d_2}$$

$$\frac{d_2 + d_1 \epsilon_r}{d_1 d_2}$$

$$\therefore \frac{\phi}{V} = \frac{\epsilon_0 \epsilon_r A}{d_2 + d_1 \epsilon_r}$$

$$\therefore \phi = V \frac{\epsilon_0 \epsilon_r A}{d_2 + d_1 \epsilon_r}$$

$$\rightarrow \text{Now, } E = \frac{k\phi}{d^2}$$

$$= \frac{1}{4\pi \epsilon_0 \epsilon_r d^2} \phi$$

$$= \frac{1}{4\pi \epsilon_0 \epsilon_r A} \frac{\phi}{d^2}$$

$$A = 4\pi d^2$$

$$\therefore d^2 = A/4\pi$$

$$\therefore E = \frac{\phi}{\epsilon_0 A \epsilon_r}$$

$$\therefore E \epsilon_0 \epsilon_r A = \phi$$

$$\therefore E \epsilon_0 \epsilon_r A = V \frac{\epsilon_0 \epsilon_r A}{d_2 + d_1 \epsilon_r}$$

$$\therefore E = \frac{V}{d_2 + d_1 \epsilon_r}$$

$$\therefore E = \frac{1000}{0.5 \times 10^{-2} + 10^{-2} \times 3}$$

$$\therefore E = \frac{1000}{3.5 \times 10^{-2}}$$

$$\therefore E = 285.7 \text{ V/m}$$