

2. A sequential circuit with Two D - flip-flops, A and B ; Two inputs x and y and One output z specified by the following next state and output equations :


$$A(t+1) = x'y + xA = DA$$

$$B(t+1) = x'B + xA = DB$$

$$Z = B.$$

- Draw the logic diagram of the circuit
- Derive the state table.
- Derive the state diagram.

→ a)

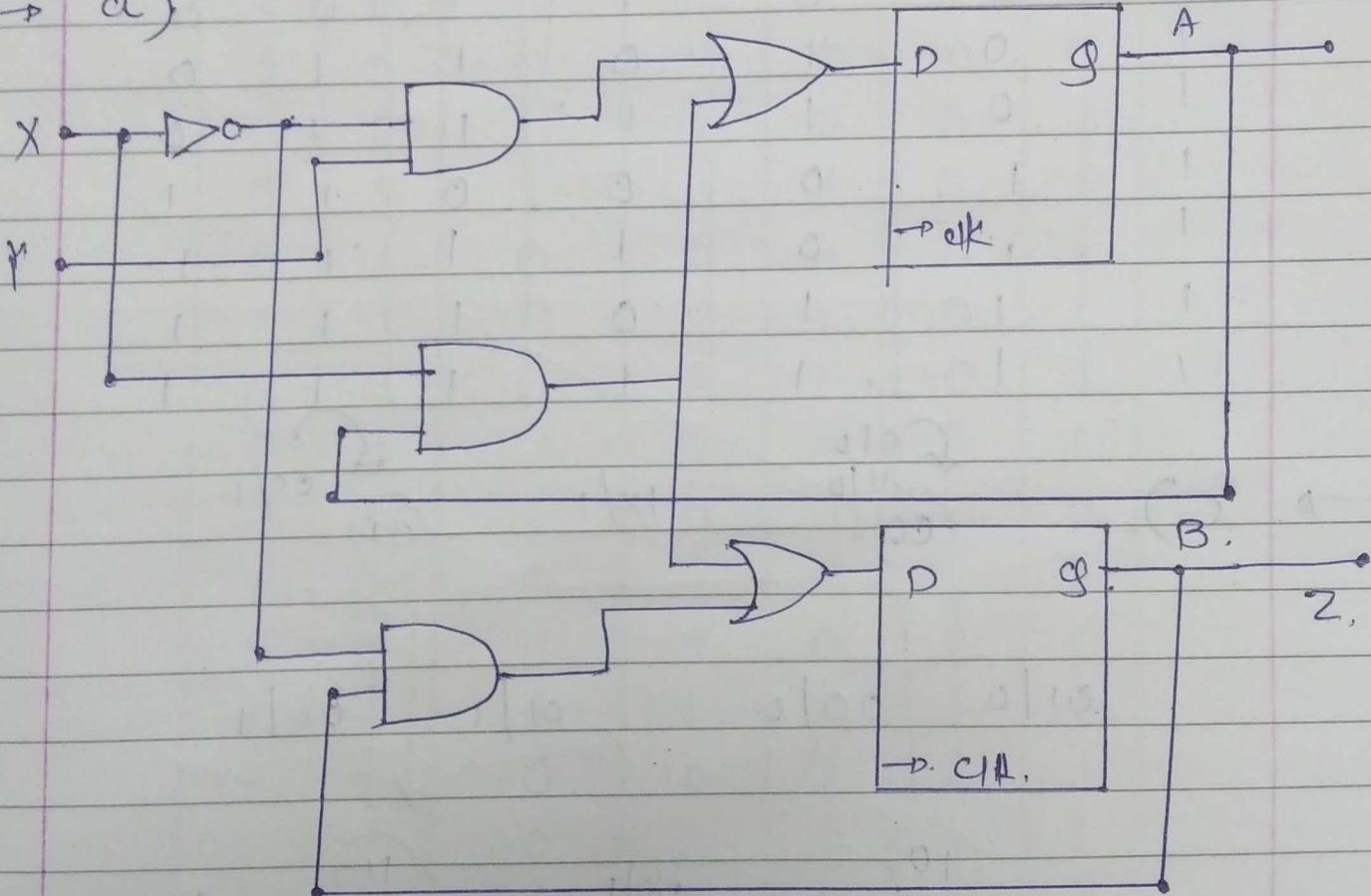


20DCS103

→ b)

Present state		Input		Next state		Output
A	B	x	y	A	B	
0	0	0	0	0	0	0
0	0	0	1	1	0	0
0	0	1	0	0	0	0
0	0	1	1	0	0	0
0	1	0	0	0	1	1
0	1	0	1	1	1	1
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	0	0	0
1	0	0	1	1	0	0
1	0	1	0	1	1	0
1	0	1	1	1	1	0
1	1	0	0	0	1	1
1	1	0	1	1	1	1
1	1	1	0	1	1	1
1	1	1	1	1	1	1

→ c)

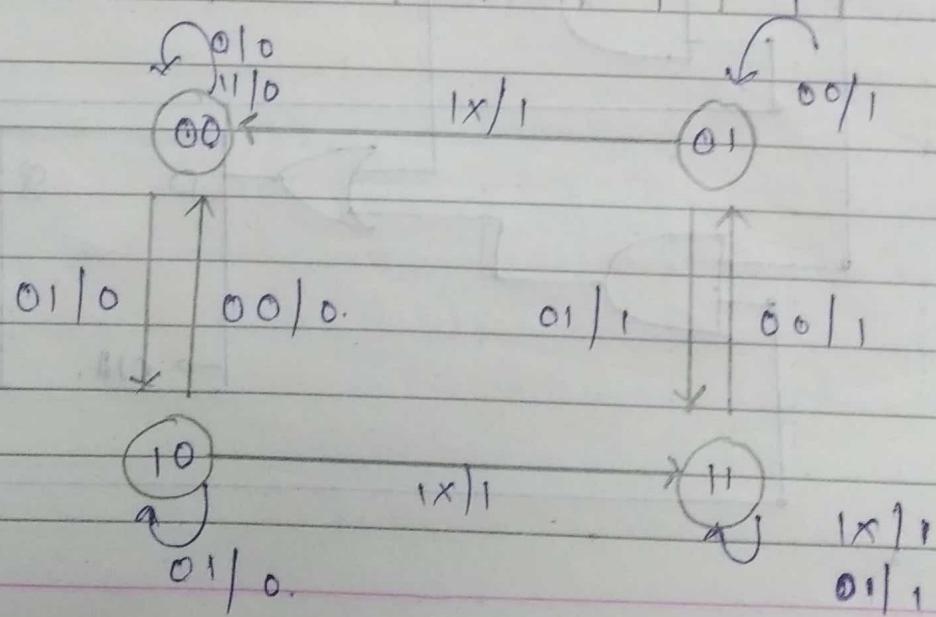

20DCS103

2. A sequential circuit has three D-flip-flops, A, B & C, and one input x . It is described by the following flip-flop input functions:

$$D_A = (Bc' + B'c)x + (Bc + B'c')\bar{x}$$

$$D_B = A$$

$$D_C = B$$


- a. Derive the state table for the circuit.
 b. Derive the state diagram.

	Present state Input				Next state		
→ a).	A	B	C	x	A	B	C
	0	0	0	0	1	0	0
	0	0	0	1	0	0	0
	0	0	1	0	0	0	0
	0	0	1	1	1	0	0
	0	1	0	0	0	0	1
	0	1	0	1	1	0	1
	0	1	1	0	1	0	1
	0	1	1	1	0	0	1
	1	0	0	0	1	1	0
	1	0	0	1	0	1	0
	1	0	1	0	0	1	0
	1	0	1	1	1	1	0
	1	1	0	0	0	1	1
	1	1	0	1	1	1	1
	1	1	1	0	1	1	1
	1	1	1	1	0	1	1


20DCS103

→ b) State diagram :-


for $x = 0$.

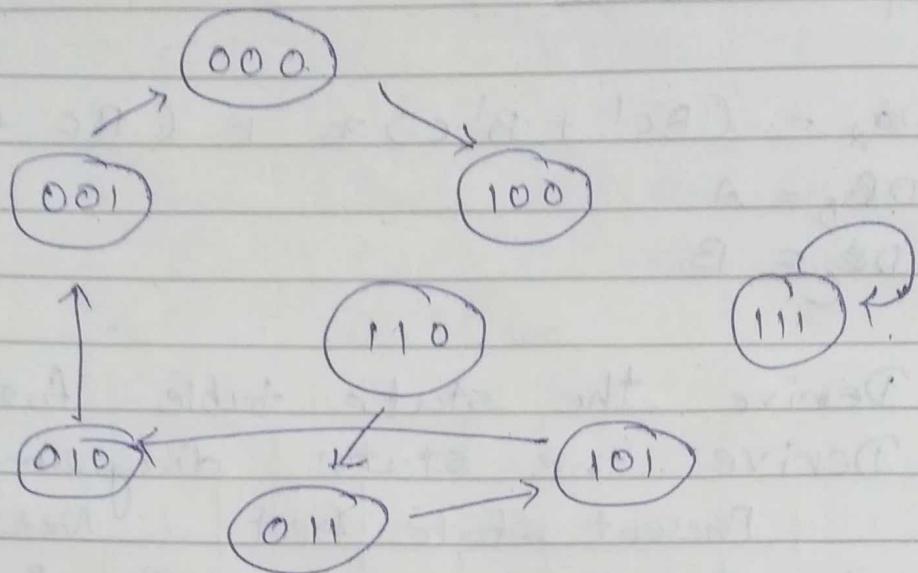

for $x = 1$.

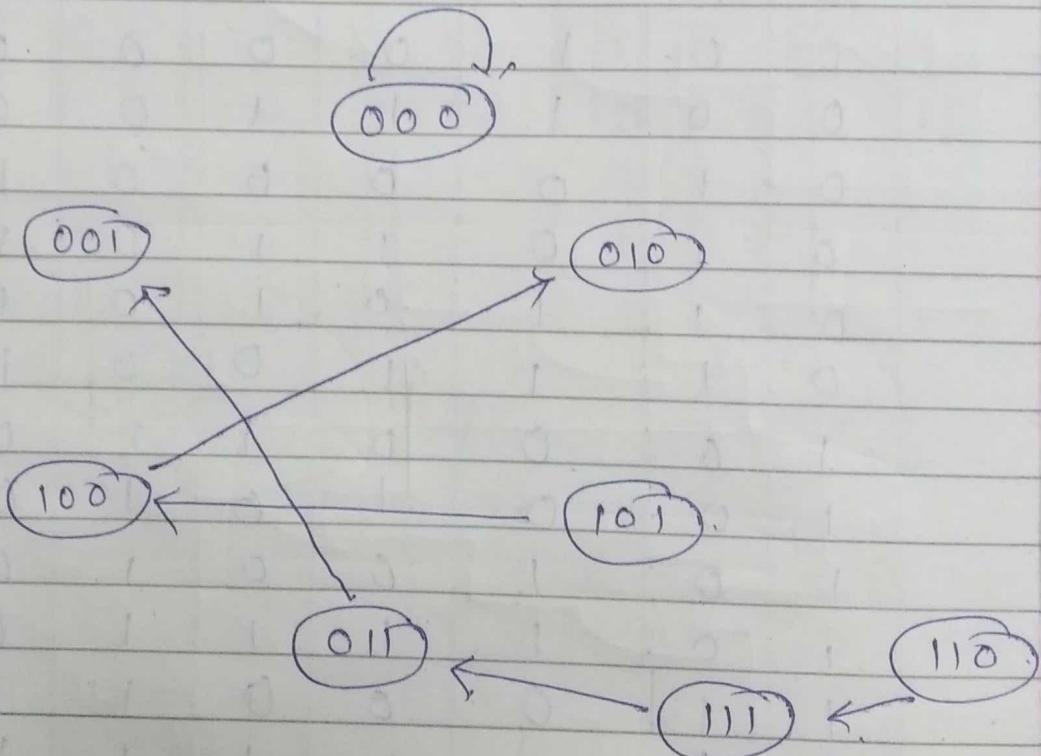

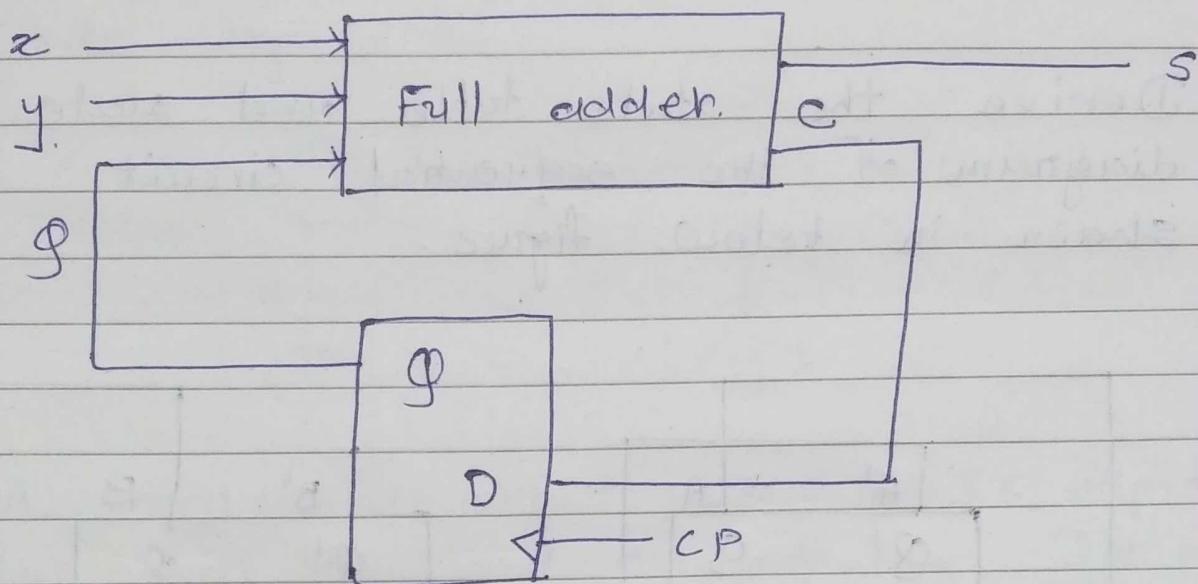
3. A sequential circuit has one flip-flop, g ; two inputs x and y and one output s . It consists of full adder circuit connected to a D-flip-flop as shown in below figure. Derive the state table and state diagram of the sequential circuit.




→ State table :-

Present state $g(t)$	Input x	y	Next state $g(t+1)$	Sum s
0 ..	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

→ State diagram :-

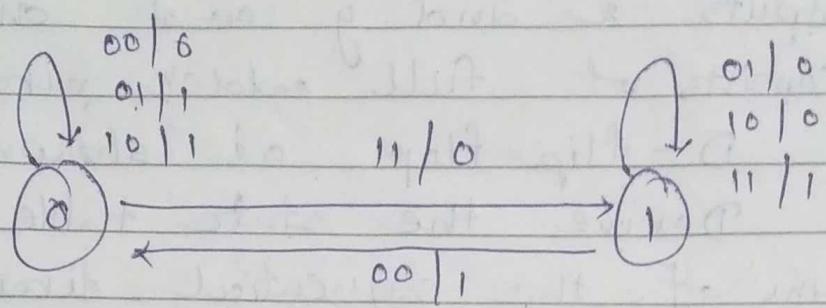

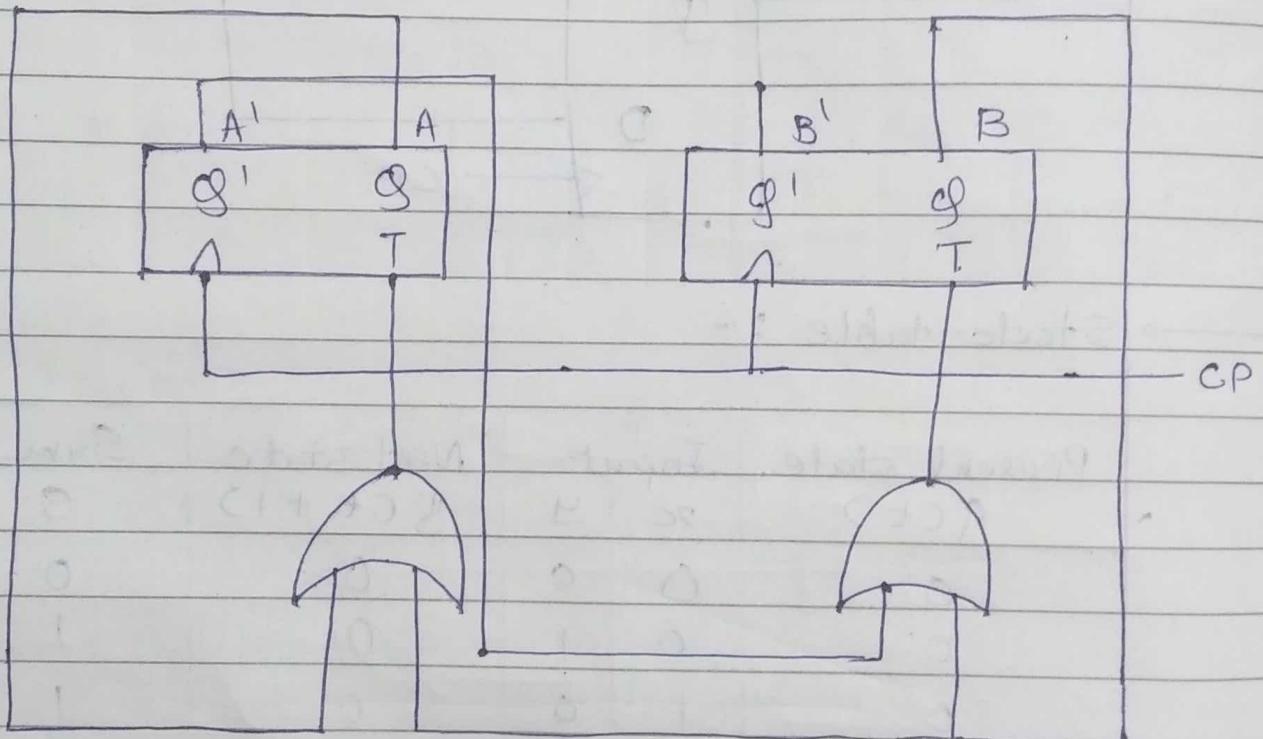4. Derive the state table and state diagram of the sequential circuit shown in below figure.




→ $T_A = A + B$


$T_B = A' + B$

Present state		Next state		Inputs	
A(t)	B(t)	A(t+1)	B(t+1)	T _A	T _B
0	0	0	1	0	1
0	1	1	0	1	1
1	0	0	0	1	0
1	1	0	0	1	1

→ State diagram :-

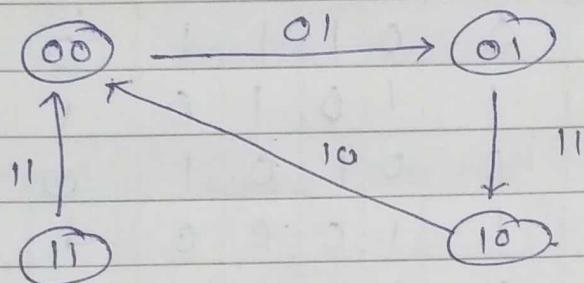

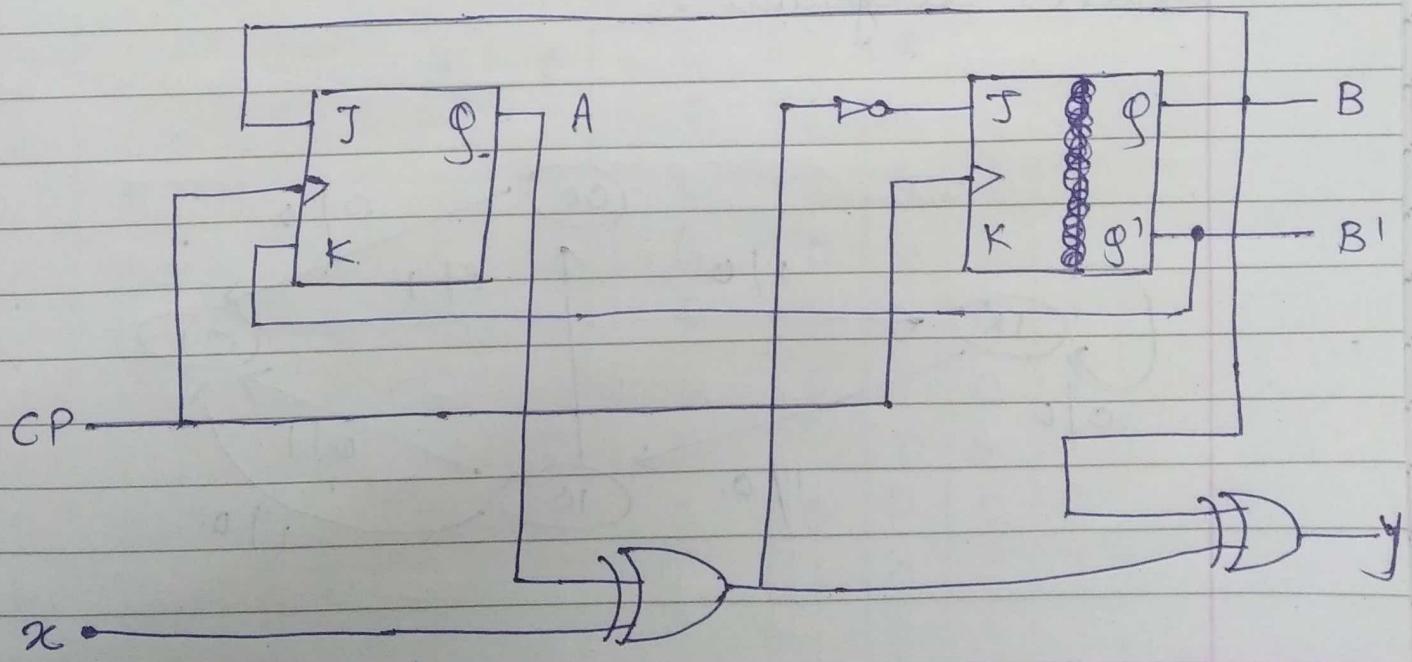Q. A sequential circuit has two JK flip-flops; one input x ; and one output y . Derive the state table and state diagram of the sequential circuit shown in below figure.



$$\rightarrow J_A = B = S_B \quad J_B = \overline{A \oplus X} = A \odot X = g_A.$$


$$K_A = \overline{B} = \overline{S_B} \quad K_B = \overline{A \oplus X} = A \odot X = g_A.$$

$$Y = B \oplus (A \oplus X).$$

→ State table :-

Input X	Present state		FF Input				Next state		Output Y
	A	B	J_A	K_A	J_B	K_B	S_A	S_B	
0	0	0	0	1	1	1	0	1	0
0	0	1	1	0	1	0	1	0	1
0	1	0	0	1	0	1	0	0	1
0	1	1	1	0	0	0	1	1	0
1	0	0	0	1	0	0	0	0	1
1	0	1	1	0	0	0	1	1	0
1	1	0	0	1	1	1	0	1	0
1	1	1	1	0	1	1	1	0	1

→ State diagram :-

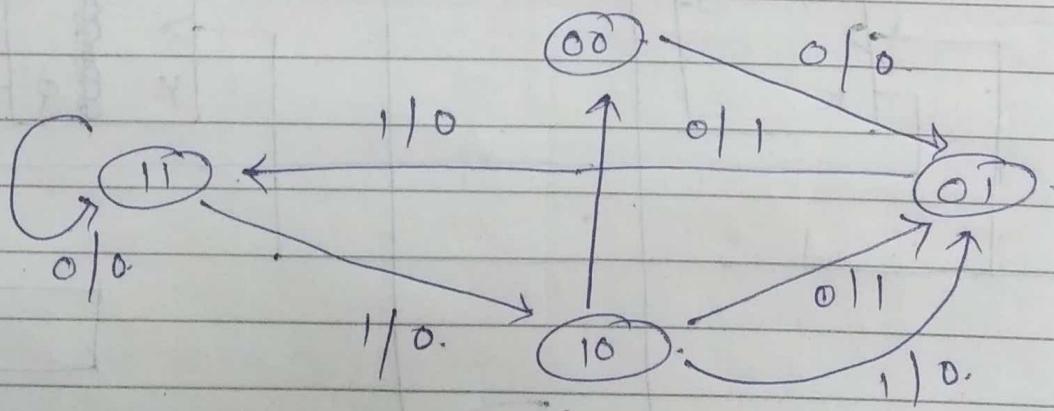

6. A sequential circuit has two JK flip-flops A and B; two inputs x and y and one output z. It is described by the following flip-flop input functions:

$$J_A = (Bx + B'y')$$

$$K_A = B'xy'$$

$$J_B = (A'x)$$

$$K_B = A + (xy')$$


$$z = (Ax'y + Bx'y')$$

a) Derive the state table for the circuit.

Present State	Input	Next state	Output	FF Input.						
A	B	x	y	A(t+1)	B(t+1)	z	J _A	K _A	J _B	K _B
0	0	0	0	1	0	0	1	0	0	0
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	1	1	0	1	1	1
0	0	1	1	0	1	0	0	0	1	0
0	1	0	0	0	1	1	0	0	0	0
0	1	0	1	0	1	0	0	0	0	0
0	1	1	0	0	1	0	1	0	1	1
0	1	1	1	1	1	0	1	0	1	0
1	0	0	0	1	0	1	1	0	0	1
1	0	0	1	1	0	0	0	0	0	1
1	0	1	0	0	0	0	1	1	0	1
1	0	1	1	1	0	0	0	0	0	1
1	1	0	0	1	0	1	0	0	0	1
1	1	0	1	1	0	0	0	0	0	1
1	1	1	0	1	0	0	1	0	0	1
1	1	1	1	1	0	0	1	0	0	1

20DCS103

→ b) State diagram :-

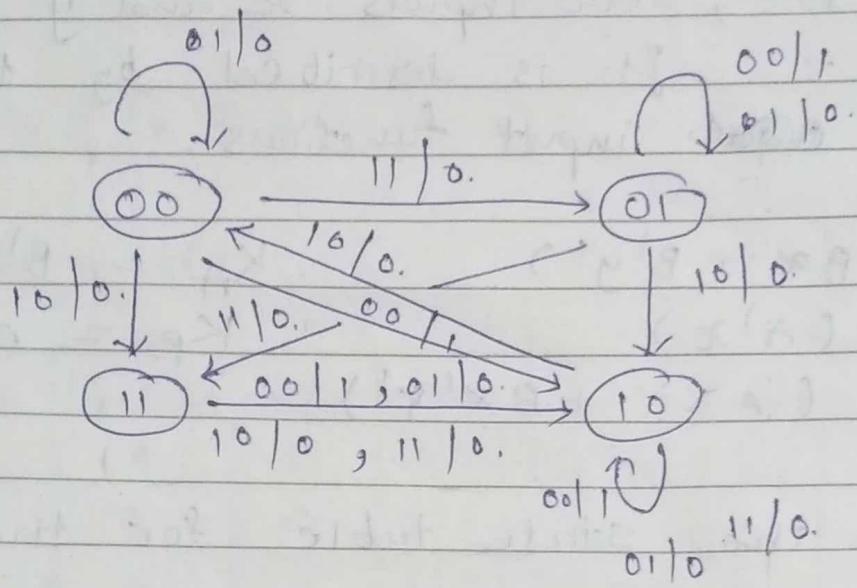

7. Draw the state diagram for the following state table. Also reduce the numbers of states of the state table. Tabulate reduced state table and draw the reduced state diagram of it.

Present State	Next State		Output	
	$x=0$	$x=1$	$x=0$	$x=1$
a	f	b	0	0
b	d	c	0	0
c	f	e	0	0
d	g	a	1	0
e	g	c	0	0
f	f	b	1	1
g	g	h	0	1
h	g	a	1	0

$$x = (d = h)$$

→ Present state | Next state | Output

Present state	$x=0$	$x=1$	$x=0$	$x=1$	
a	f	b	0	0	
b	h	c	0	0	
c	f	e	0	0	
d	g	a	1	0	
e	h	c	0	0	$x(b=e)$
f	g	h	1	1	
g	g	a	0	1	


→ Present state | Next state | Output

Present state	$x=0$	$x=1$	$x=0$	$x=1$	
a	f	b	0	0	
b	h	c	0	0	
c	f	b	0	0	$x(c=0)$
d	g	a	1	0	
f	g	h	1	1	
g	g	a	0	1	


→ Present state | Next state | Output

Present state	$x=0$	$x=1$	$x=0$	$x=1$	
a	f	b	0	0	
b	h	c	0	0	
d	g	a	1	0	
f	g	h	1	1	
g	g	a	0	1	

→ State diagram :-

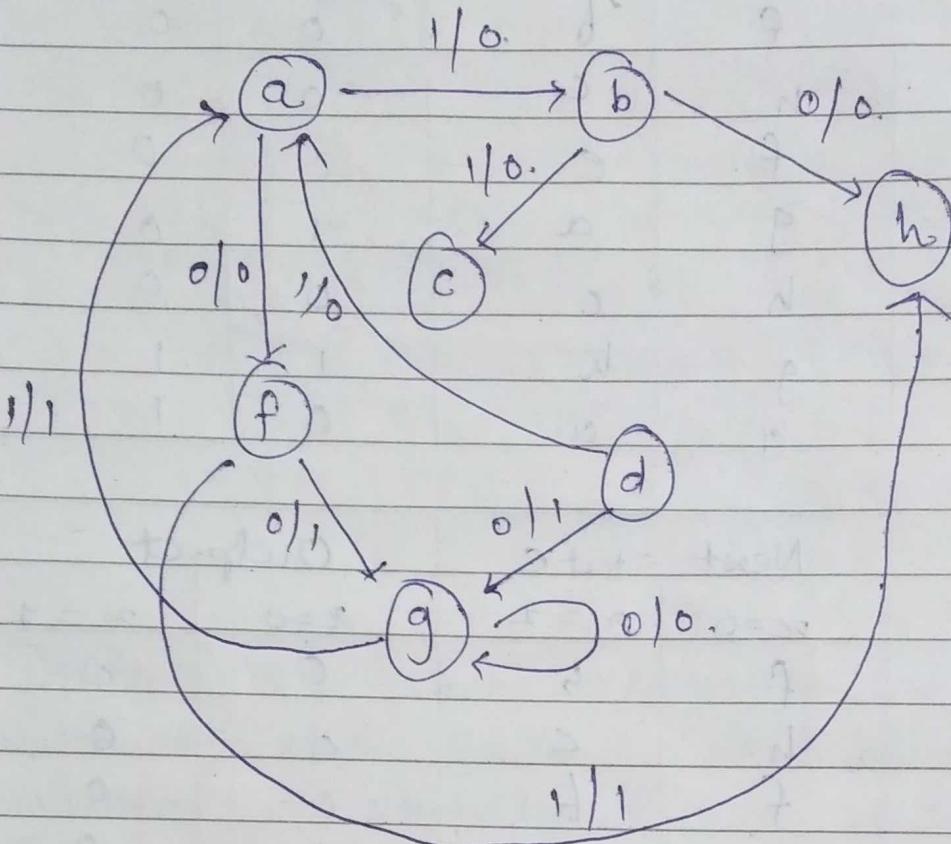

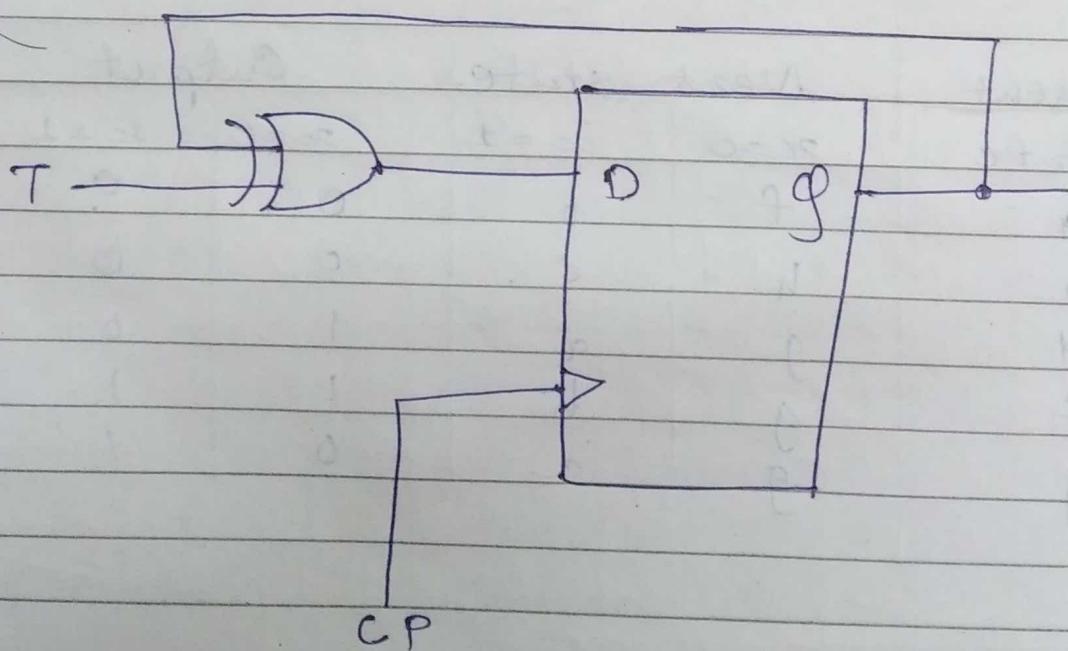8. Analyze the circuit shown below and prove that it is equivalent to a T-flip flop



From the circuit, we can write that,

$$D = T \oplus Q$$

D	Q_{n+1}
0	0
1	1

Suppose, initially Q_n is set to 0, and $T = 0$.

$$\begin{aligned} \therefore D &= Q \oplus T \\ &= 0 \oplus 0 \\ &= 0 \end{aligned}$$

$$\begin{aligned} \text{Thus, } Q_{n+1} &= 0 \\ &= Q_n. \end{aligned}$$

Suppose $Q_n = 0$ and $T = 1$.

$$\begin{aligned} \therefore D &= Q \oplus T \\ &= 0 \oplus 1 \\ &= 1 \end{aligned}$$

$$\text{Thus, } Q_{n+1} = \bar{Q}_n$$

when $T = 0$, $Q_{n+1} = Q_n$

and $T = 1$, $Q_{n+1} = \bar{Q}_n$

T	Q_{n+1}
0	Q_n
1	\bar{Q}_n

$$, Q_{n+1} = T \oplus Q_n$$

Hence, it proved as T-flip flop.

20DCS103

Q. Design a sequential circuit with two JK flip-flops A and B and two inputs E and X. If $E=0$, the circuit remains in the same state regardless of input X . When $E=1$ and $X=1$, the circuit goes through the state transitions from 00 to 01 to 10 to 11 back to 00 and repeats. When $E=1$ & $X=0$, the circuit goes through the state transitions from 00 to 11 to 10 to 01 back to 00 and repeats.

→ When $E=0$, Next state = Present state

when $E=1$ & $X=1$

Transitions : $00 \rightarrow 01$
 $01 \rightarrow 10$
 $10 \rightarrow 11$
 $11 \rightarrow 00$.

when $E=1$ & $X=0$

Transitions : $00 \rightarrow 11$
 $11 \rightarrow 10$
 $10 \rightarrow 01$
 $01 \rightarrow 00$.

Present state	Inputs			Next state		FF		Outputs		
	A	B	E	X	A(t+1)	B(t+1)	J _A	K _A	J _B	K _B
0 0	0 0	0 0	0 0	0 0	0 0	0 0	0 0	X 0	0 X	X
0 0	0 0	0 0	1 1	0 0	0 0	0 0	0 0	X 0	0 X	X
0 0	0 0	1 0	0 0	1 1	1 1	1 1	X 1	1 X	1 X	X
0 0	0 0	1 1	1 1	0 0	1 1	0 1	0 X	1 1	1 X	X
0 1	0 1	0 0	0 0	0 0	1 0	0 1	0 X	X X	0 0	0
0 1	0 1	0 1	0 1	0 0	1 0	0 1	0 X	X X	0 0	0
0 1	1 1	0 0	0 0	0 0	0 0	0 0	0 X	X X	1 1	1
0 1	1 1	1 1	1 1	1 1	0 0	1 0	X X	X X	1 1	1
1 0	0 0	0 0	0 0	1 1	0 0	X 0	0 0	0 0	X X	X
1 0	0 0	0 1	1 1	0 0	0 0	X 0	0 0	0 0	X X	X
1 0	1 0	0 0	0 0	0 0	1 1	X 1	1 1	1 X	1 X	X
1 0	1 0	1 1	1 1	1 1	1 1	X 0	0 1	1 X	1 X	X
1 1	0 0	0 0	1 1	1 1	1 1	X 0	0 X	X 0	0 0	0
1 1	0 1	1 1	1 1	1 1	1 1	X 0	0 X	0 X	0 0	0
1 1	1 0	1 0	1 1	0 0	0 0	X 0	0 X	X 1	1 X	1
1 1	1 1	1 1	1 1	0 0	0 0	X 1	1 X	1 X	1 X	1

→ K-map for J_A :

AB \ EX		00	01	11	10
00	0 0	0 0	0 0	(1)	
01	0 0	0 0	1 0	0	
11	X X	X X	X X	X X	
10	X X	X X	X X	X X	

$$J_A = BEX + B^1EX^1$$

20DCS103

$$\therefore J_A = E(BX + B'X')$$

$$= E(B \oplus X)$$

→ K-map for K_A :

AB \ EX	00	01	11	10
00	X	X	X	X
01	X	X	X	X
11	0	0	1	0
10	0	0	0	1

$$\therefore K_A = E(B \oplus X)$$

→ K-map for J_B :


AB \ EX	00	01	11	10
00	0	0	1	1
01	X	X	X	X
11	X	X	X	X
10	0	0	1	1

$$\therefore J_B = E.$$

\rightarrow K-map for K_B :

AB \ EX	00	01	11	10
00	X	X	X	X
01	0	0	1	1
11	0	0	1	1
10	X	X	X	X


$$\therefore K_B = E$$

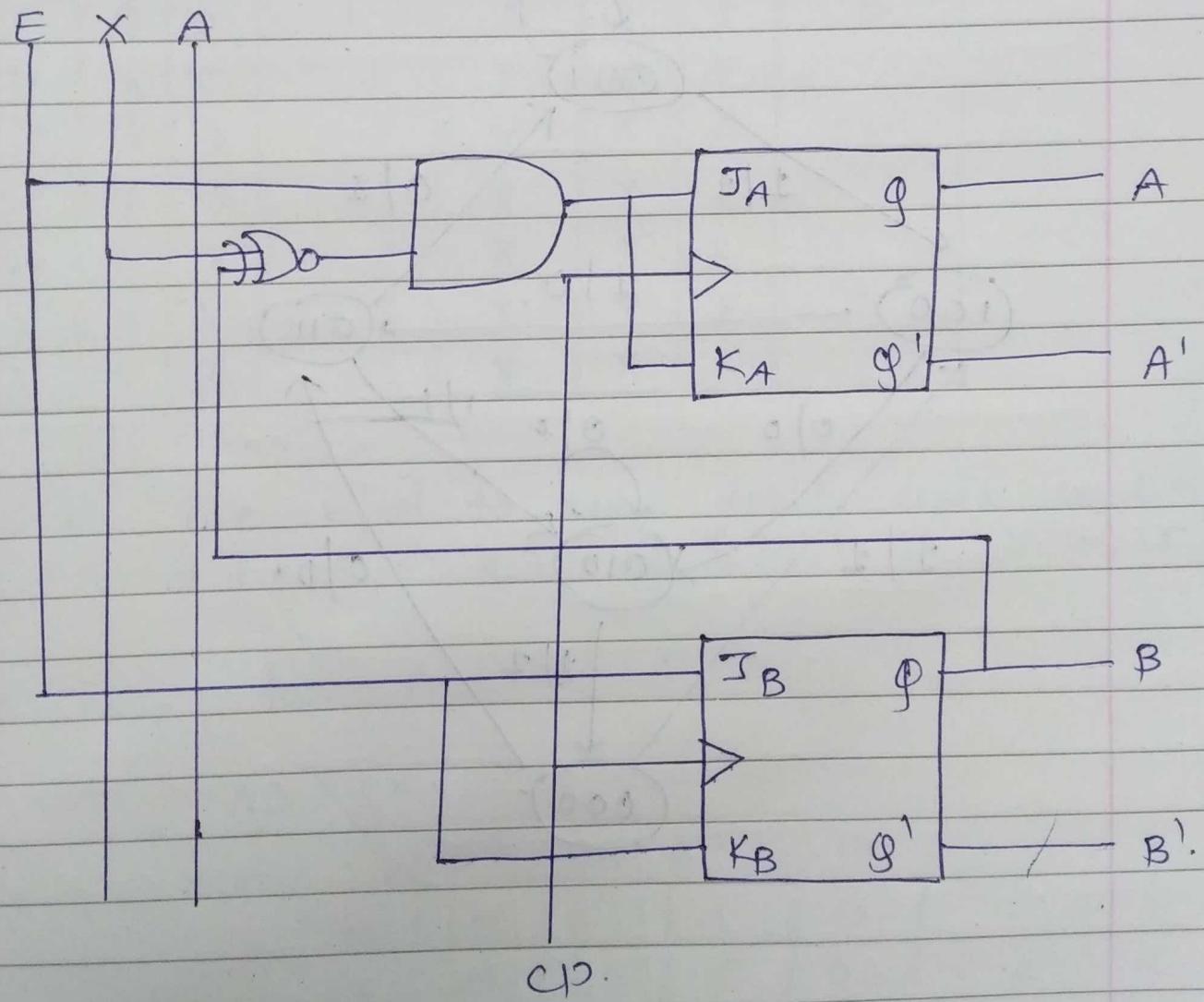

10. A sequential circuit has three flip-flops A, B and C. One input ~~X~~ X and one output Y. The state diagram is as shown below.

- Design the sequential circuit using D flip-flops
- Design the sequential circuit using JK-Flip-flops.

Consider unused state as don't care.

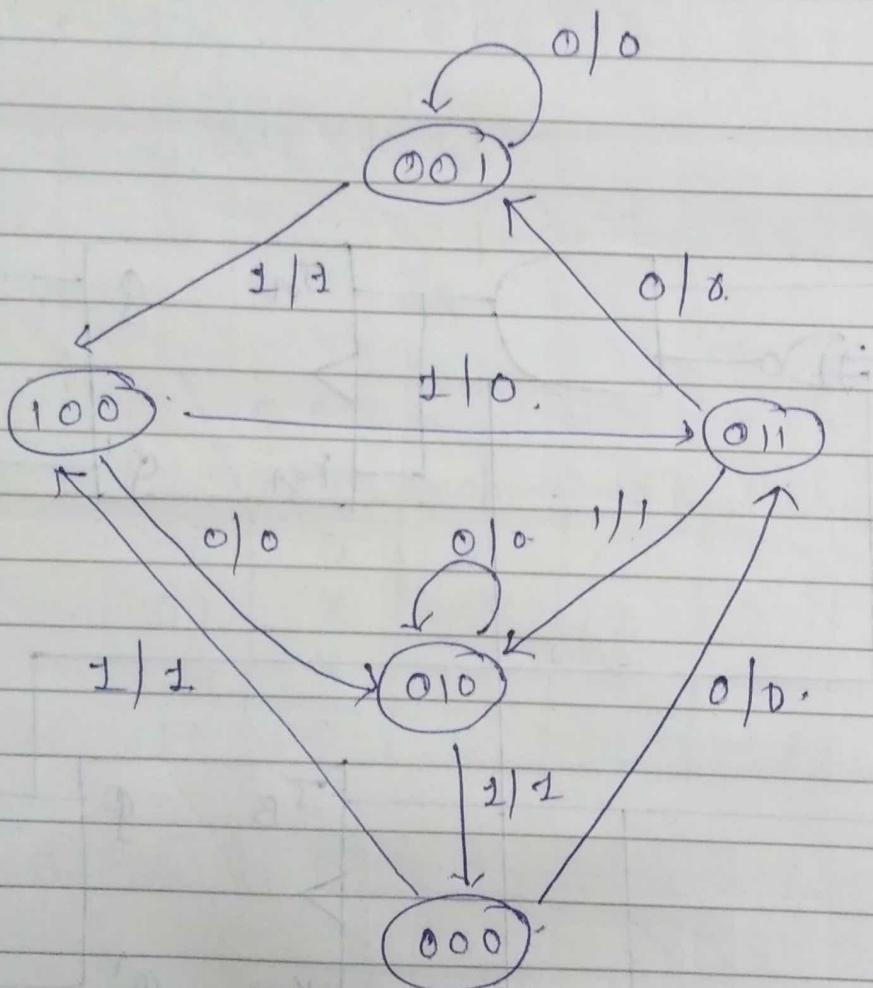

Present State Input				Next State		Output	
A	B	C	X	A(t+1)	B(t+1) C(t+1)	Y	
0	0	0	0	0	1	1	0
0	0	0	1	1	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	1	0	0	1
0	1	0	0	0	1	0	0
0	1	0	1	0	0	0	1
0	1	1	0	0	0	1	0
0	1	1	1	0	1	0	1
1	0	0	0	0	1	0	0
1	0	0	1	0	1	1	0
x	x	x		x	x	x	
x	x	x		x	x	x	
x	x	x		x	x	x	
x	x	x		x	x	x	
x	x	x		x	x	x	

→ Now, we need to use don't care condition
 i.e. $d(A, B, C, x) = \Sigma (10, 11, 12, 13, 14, 15)$.

→ K-map for $A(t+1)$:

AB \ CX	00	01	10	11
00	0	1	1	0
01	0	0	0	0
11	x	x	x	x
10	0	0	x	x

$= A' B' x = PA'$

→ K-map for $B(t+1)$:

AB \ CX

	00	01	11	10
00	1	0	0	0
01	1	0	01	0.
11	X	X	X	X
10	1	1	X	X

$$\begin{aligned}
 &= A + C'X' + \\
 &= BCX \\
 &= DB.
 \end{aligned}$$

→ K-map for $C(t+1)$:

AB \ CX

	00	01	11	10
00	1	0	0	1
01	0	0	0	1
11	X	X	X	X
10	0	1	X	X

$$\begin{aligned}
 &= AX + CX' + \\
 &= A' B' X' \\
 &= DC.
 \end{aligned}$$

→ K-map for Y_e :


AB \ CX

	00	01	11	10
00	0	1	1	0
01	0.	1	1	0
11	X	X	X	X
10	0	0	X	X

$$= A'x = D!$$

20DCS103

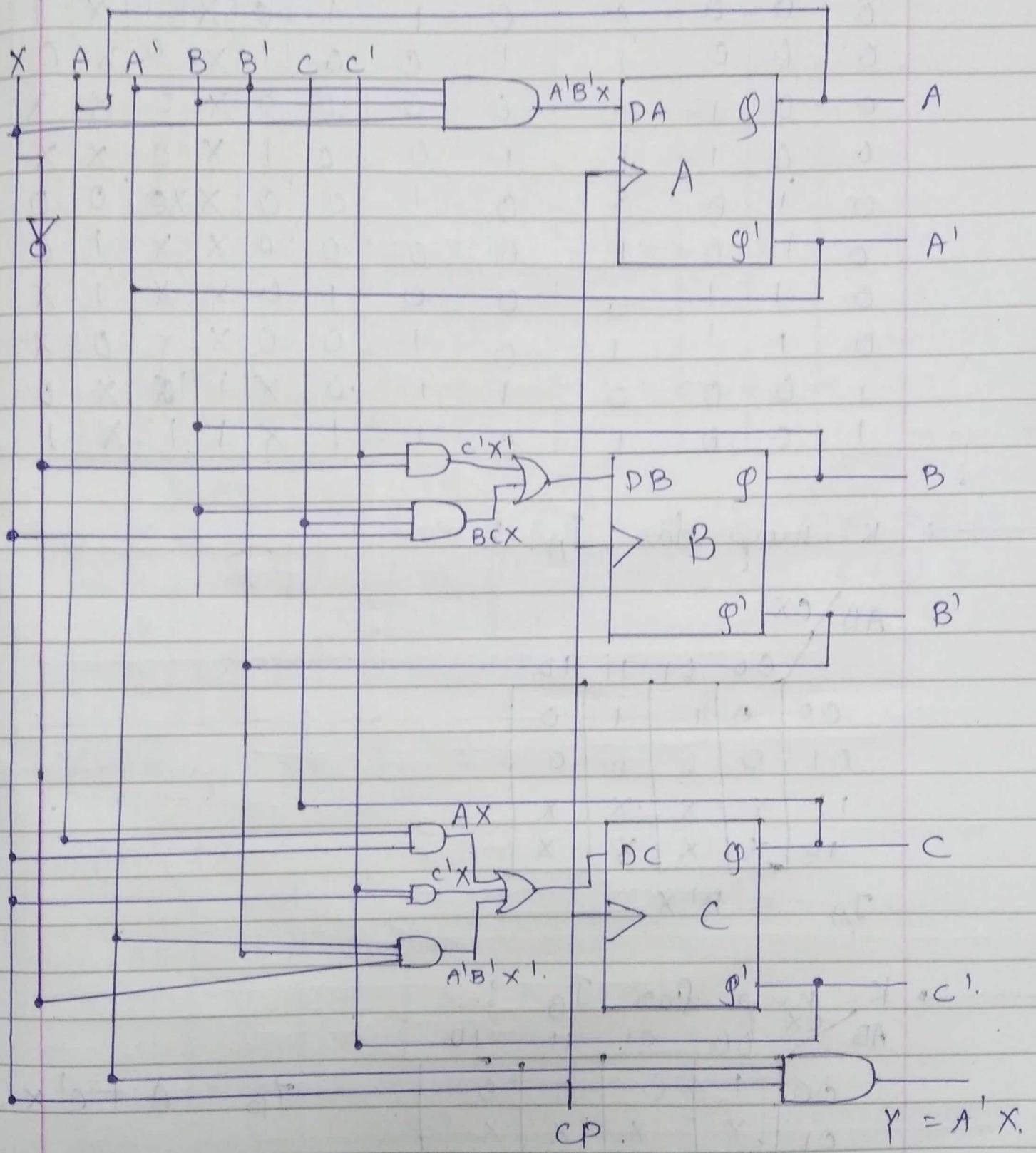• Sequential circuit using D- flip-flops.



20DCS103

Present state			Input	Next state.			FF. Input.						
A	B	C	X	A(t+1)	B(t+1)	C(t+1)	J _A	K _A	J _B	K _B	J _C	K _C	
0	0	0	0	0	1	1	0	X	1	X	1	X	
0	0	0	1	1	0	0	1	X	0	X	0	X	
0	0	1	0	0	0	1	0	X	0	X	X	0	
0	0	1	1	1	0	0	0	1	X	0	X	X	
0	1	0	0	0	1	0	0	0	X	0	0	X	
0	1	0	1	0	0	0	0	0	X	X	1	0	X
0	1	1	0	0	0	1	0	X	X	1	X	0	
0	1	1	1	0	1	0	0	0	X	X	0	X	
1	0	0	0	1	1	0	X	1	1	X	0	X	
1	0	0	1	0	1	1	X	1	1	X	1	X	

→ K-map for J_A:

AB \ CX	00	01	11	10
00	0	1	1	0
01	0	0	0	0
11	X	X	X	X
10	X	X	X	X

$$J_A = B' X$$

→ K-map for J_B:

AB \ CX	00	01	11	10
00	1	0	0	0
01	X	X	X	X
11	X	X	X	X
10	1	1	X	X

$$J_B = A + C' X$$

20DCS103

→ K-map for k_A :

AB \ CX

	00	01	11	10
00	X	X	X	X
01	X	X	X	X
11	X	X	X	X
10	1	1	X	X

$$k_A = 1$$

→ K-map for k_B :

AB \ CX

	00	01	11	10
00	X	X	X	X
01	0	1	0	1
11	X	X	X	X
10	X	X	X	X

$$\begin{aligned} k_B &= c'x + cx' \\ &= c \oplus x \end{aligned}$$

→ K-map for J_C :

AB \ CX

	00	01	11	10
00	1	0	X	X
01	0	0	X	X
11	X	X	X	X
10	0	1	X	X

$$J_C = Ax + A'B'C'$$

→ K-map for K_C :


$AB \backslash CX$

	00	01	11	10
00	X	X	1	0
01	X	X	1	0
11	X	X	X	X
10	X	X	X	X

$$K_C = X.$$

$$Y = A'X.$$

→ Sequential circuit using JK flipflop:

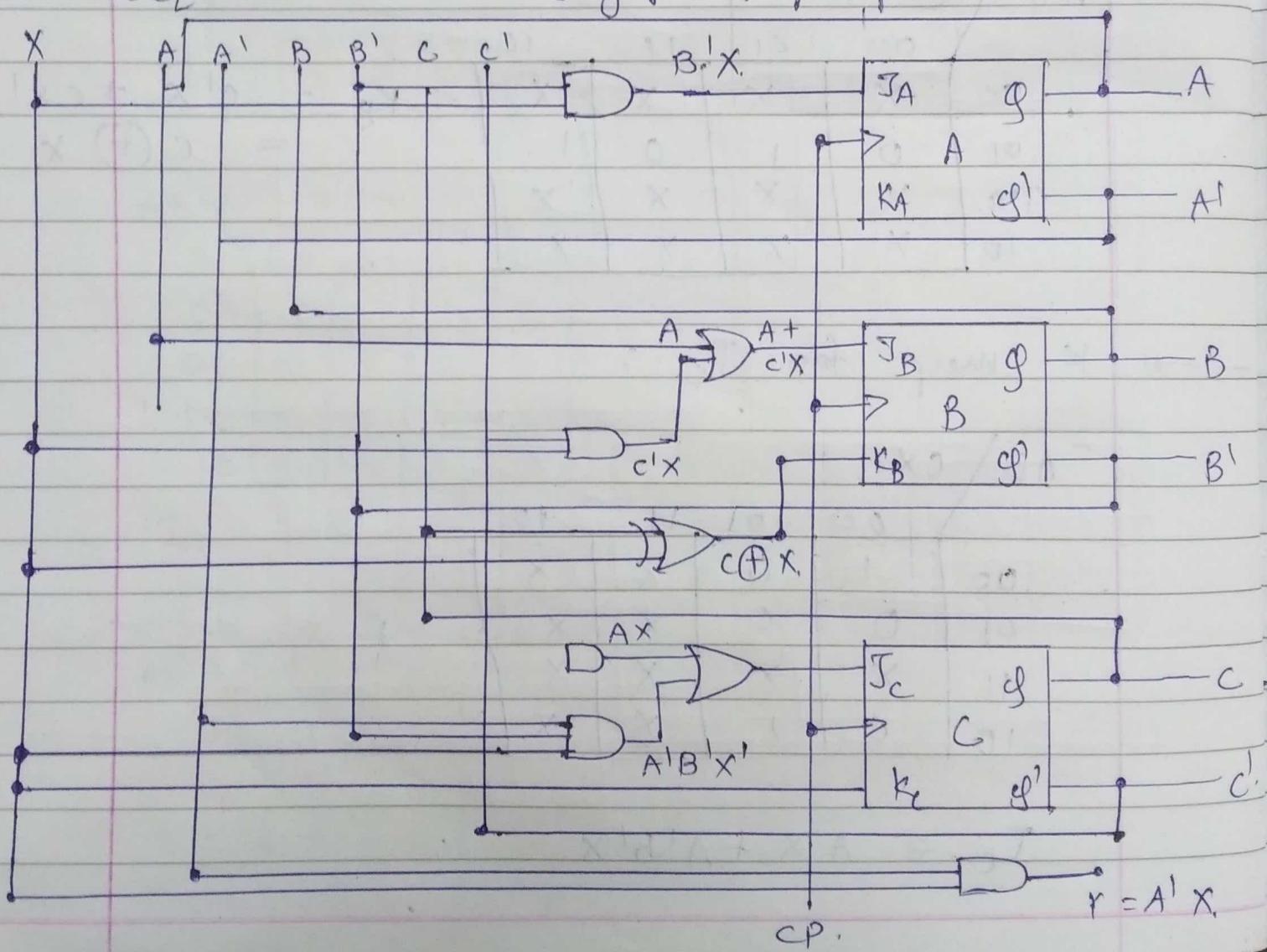

II. Design 4-bit binary counter using JK flip flop.

→ Number of digits = $N = 4$.

Number of FF CN = 2.

Present state				Next state				FF Inputs							
A	B	C	D	A (C+D)	B (C+D)	C (C+D)	D (C+D)	J _A	K _A	J _B	K _B	J _C	K _C	J _D	K _D
0	0	0	0	0	0	0	1	0	X	0	X	0	X	1	X
0	0	0	1	0	0	1	0	0	X	0	X	1	X	X	1
0	0	1	0	0	0	1	1	0	X	0	X	X	0	1	X
0	0	1	1	0	1	0	0	0	X	1	X	X	1	X	1
0	1	0	0	1	0	1	0	1	0	X	X	0	0	X	1
0	1	0	1	0	1	1	0	0	X	X	0	1	X	X	1
0	1	1	0	0	1	1	1	0	X	X	0	X	0	1	X
0	1	1	1	1	0	0	0	1	X	X	1	X	1	X	1
1	0	0	0	1	0	0	1	X	0	0	X	0	X	1	X
1	0	0	1	0	0	0	0	X	1	0	X	0	X	X	1
1	0	1	0	0	0	0	0	X	1	0	X	X	1	0	X
1	0	1	1	0	0	0	0	X	1	0	X	X	1	X	1
1	1	0	0	0	0	0	0	X	1	X	1	0	X	0	X
1	1	0	1	0	0	0	0	X	1	X	1	0	X	X	1
1	1	1	0	0	0	0	0	X	1	X	1	X	1	0	X
1	1	1	1	0	0	0	0	X	1	X	1	X	1	X	1

→ K map for J_A:

AB	CD			
	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	X	X	X	X
10	X	X	X	X

$$J_A = BCD.$$

20DCS103

→ K map for K_A :

$$K_A = B + D + C$$

		AB \ CD	00	01	11	10
		00	X	X	X	X
		01	X	X	X	X
		11	1	1	1	1
		10	0	1	1	1

→ K map for J_B and for K_B

		AB \ CD	00	01	11	10
		00	0	0	1	0
		01	X	X	X	X
		11	X	X	X	X
		10	0	0	0	0

		AB \ CD	00	01	11	10
		00	X	X	X	X
		01	0	0	1	0
		11	1	1	1	1
		10	1	X	X	0

$$J_B = \bar{A}CD$$

$$K_B = CD + A$$

→ K map for J_C and for K_C .

		AB \ CD	00	01	11	10
		00	0	1	X	X
		01	0	1	X	X
		11	0	0	X	X
		10	0	0	X	X

		AB \ CD	00	01	11	10
		00	X	X	1	0
		01	X	X	1	0
		11	X	X	1	1
		10	X	X	1	1

$$J_C = \bar{A}D$$

$$K_C = D + A$$


→ K-map for I_D and for K_D

AB	CD	00	01	11	10
00		1	X	X	1
01		1	X	1	1
11		0	X	X	0
10		1	X	X	0


AB	CD	00	01	11	10
00		X	1	1	X
01		X	1	1	X
11		X	1	1	1
10		X	1	1	1

$$I_D = \bar{A} + \bar{B}\bar{C}$$

$$K_D = 1.$$

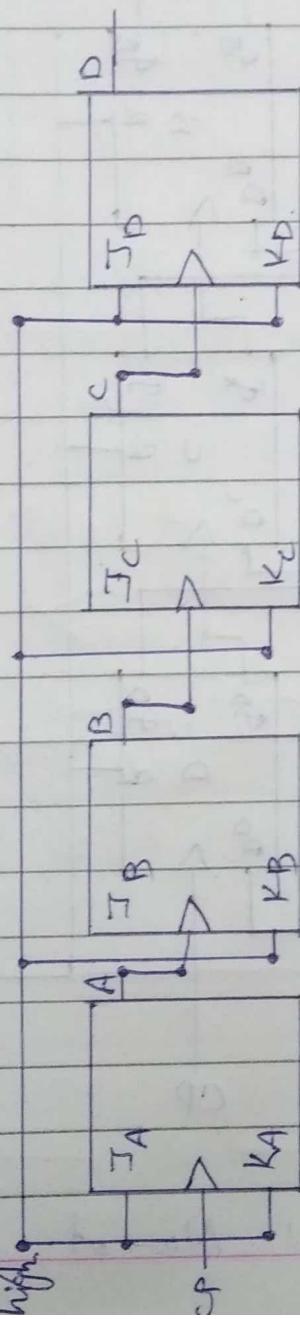

12. Design BCD counter using D-Hip-flop.

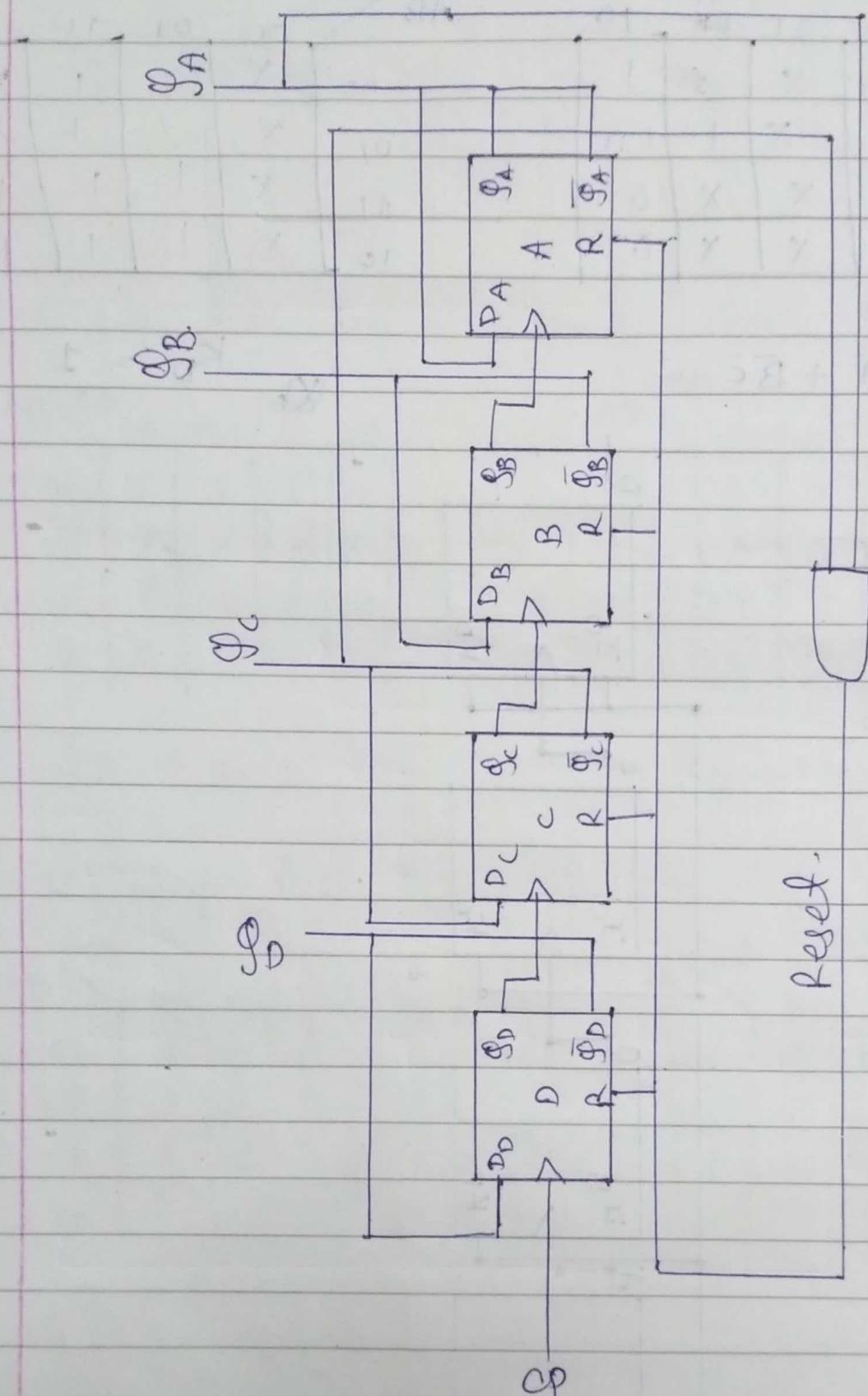

Ref.

$$\rightarrow 2^n \geq N = 10.$$

$$2^4 \geq 16 > 10. \therefore \text{No. of Flip-flop} = 4.$$

20DCS103



13. Design mod-4 counter using T-Slip-flop.

$$\rightarrow \text{Number of flip-flops} = 2^n \\ = 2^1 = 2.$$

$N = 0$ (for up), $N = 1$ (for sum).


Present state		Next state		FF Outputs	
A	B	A(t+1)	B(t+1)	T _A	T _B
0	0	0	1	0	1
0	1	1	0	1	1
0	1	0	0	0	1
0	0	1	1	1	1
1	0	1	1	0	1
1	1	0	0	1	1
1	1	1	0	0	1
1	0	0	1	1	1

→ K-map for T_A: → K-map for T_B:

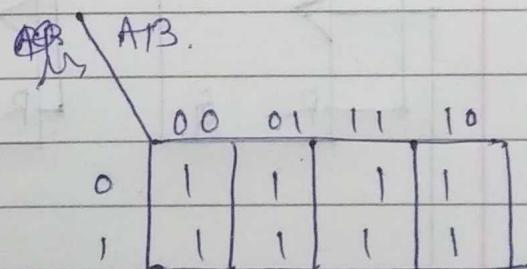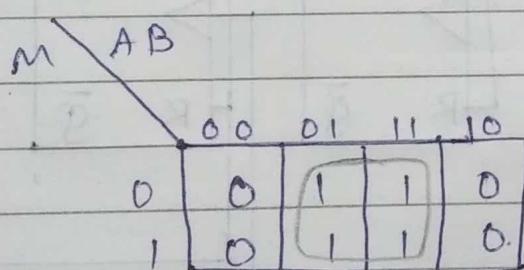


$$T_A = B$$

$$T_B = 1.$$

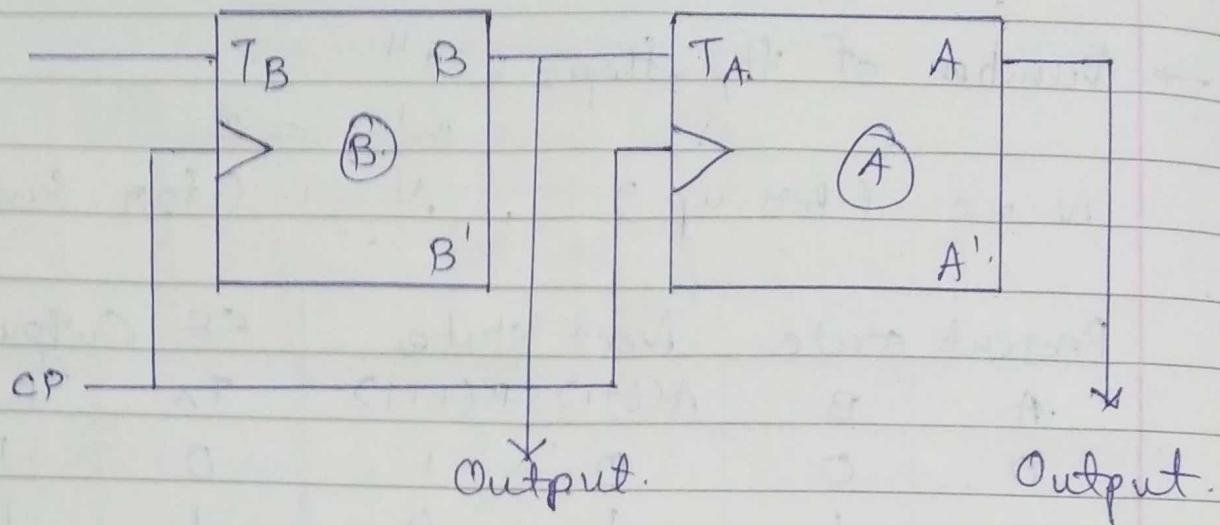

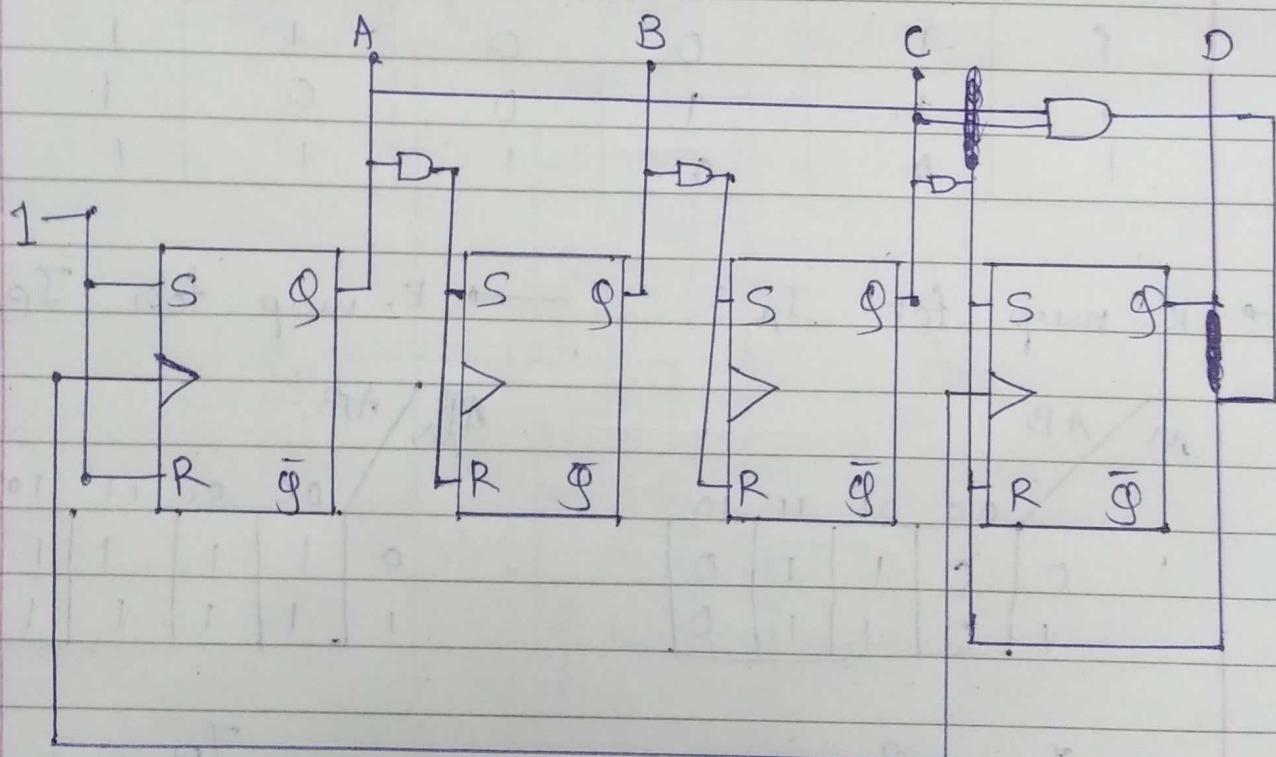14. Design decimal counter using SR flip-flop.



→ X →